

Making integrated circuits

2013-04-10, Carsten Wulff

Topic for today

- How do we make integrated circuits
- What to focus on the next five years

Who am I

- Carsten Wulff
- Born friday 13. August 1976
- Senior R & D engineer at Nordic Semiconductor
- Married with three kids
- Master (2002), Ph.D (2008)

What do I do?

Analog integrated circuit design,
mostly analog to digital
converters



nRF51822

Multiprotocol *Bluetooth® 4.0 low energy/2.4 GHz RF SoC*

Product Specification v1.1

Key Features

- 2.4 GHz transceiver
 - -93 dBm sensitivity *Bluetooth® low energy*
 - 250 kbps, 1 Mbps, 2 Mbps supported data rates
 - TX Power -20 to +4 dBm in 4 dB steps
 - TX Power -30 dBm Whisper mode
 - 13 mA peak RX, 10.5 mA peak TX (0 dBm)
 - RSSI (1 dB resolution)
- ARM® Cortex™-M0 32 bit processor
 - 275 µA/MHz running from flash memory
 - 150 µA/MHz running from RAM
 - Serial Wire Debug (SWD)
- S100 series SoftDevice ready
- Memory
 - 256 kB or 128 kB embedded flash program memory
 - 16 kB RAM
- Support for non-concurrent multiprotocol operation
 - On-air compatibility with nRF24L series
- Flexible Power Management
 - Supply voltage range 1.8 V to 3.6 V
 - 2.5 µs fast wake-up using 16 MHz RCOSC
 - 0.4 µA @ 3 V OFF mode
 - 0.5 µA @ 3 V in OFF mode + 1 region RAM retention
 - 2.3 µA @ 3 V ON mode, all blocks IDLE
- 8/9/10 bit ANC - 8 configurable channels
- 31 General Purpose I/O Pins
- Two 16 bit and one 32 bit timers with counter mode
- SPI Master

Applications

- Computer peripherals and
 - Mouse
 - Keyboard
 - Multi-touch
- Interactive entertainment
 - Remote control
 - 3D Glasses
 - Gaming console
- Personal Area Networks
 - Health and fitness monitors
 - Medical devices
 - Key-fobs + tags
- Remote control toys


**How do we make
integrated circuits?**

Transistor

1947: First transistor




1958: Integrated circuit

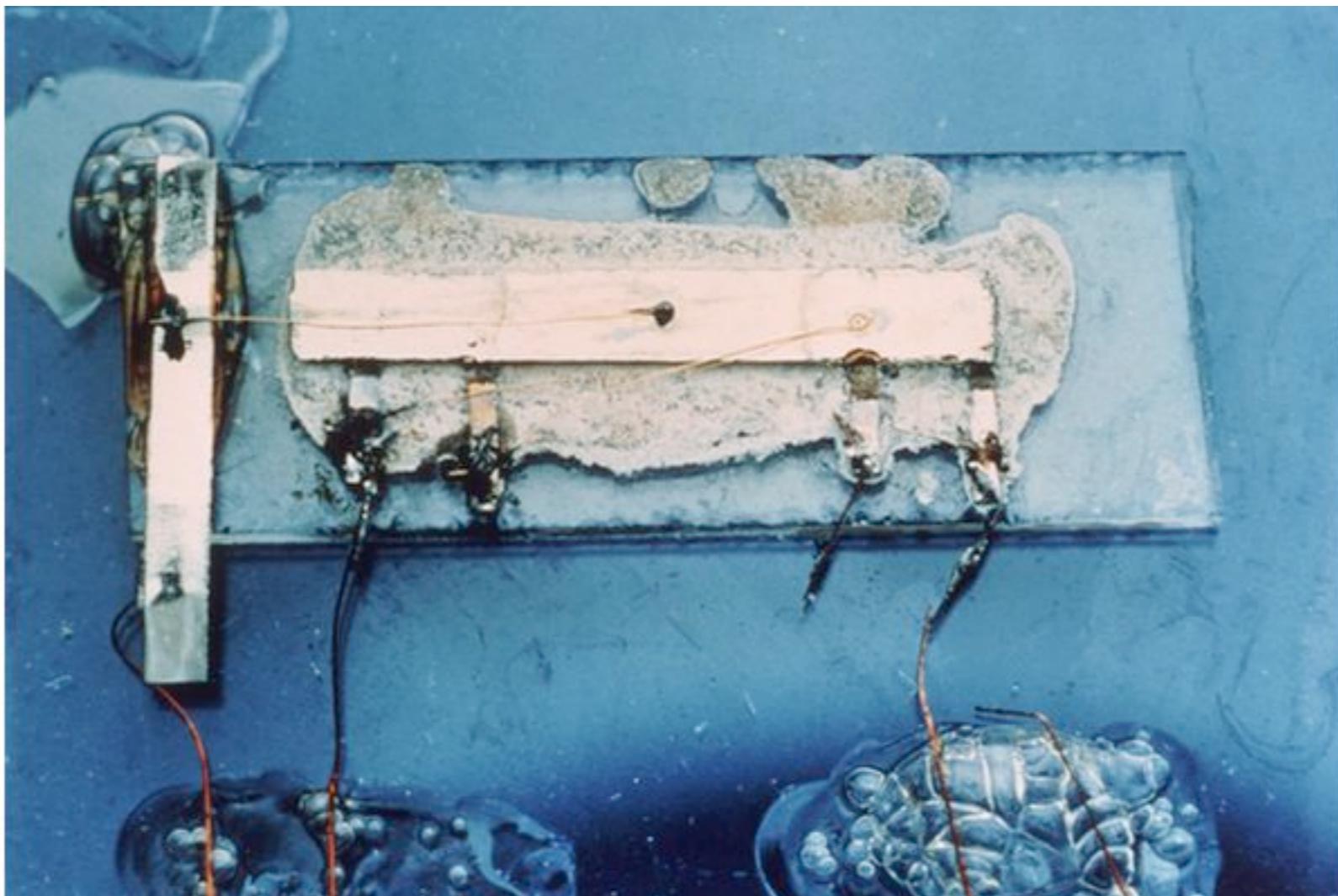

http://en.wikipedia.org/wiki/Jack_Kilby


2012: Virtex-7

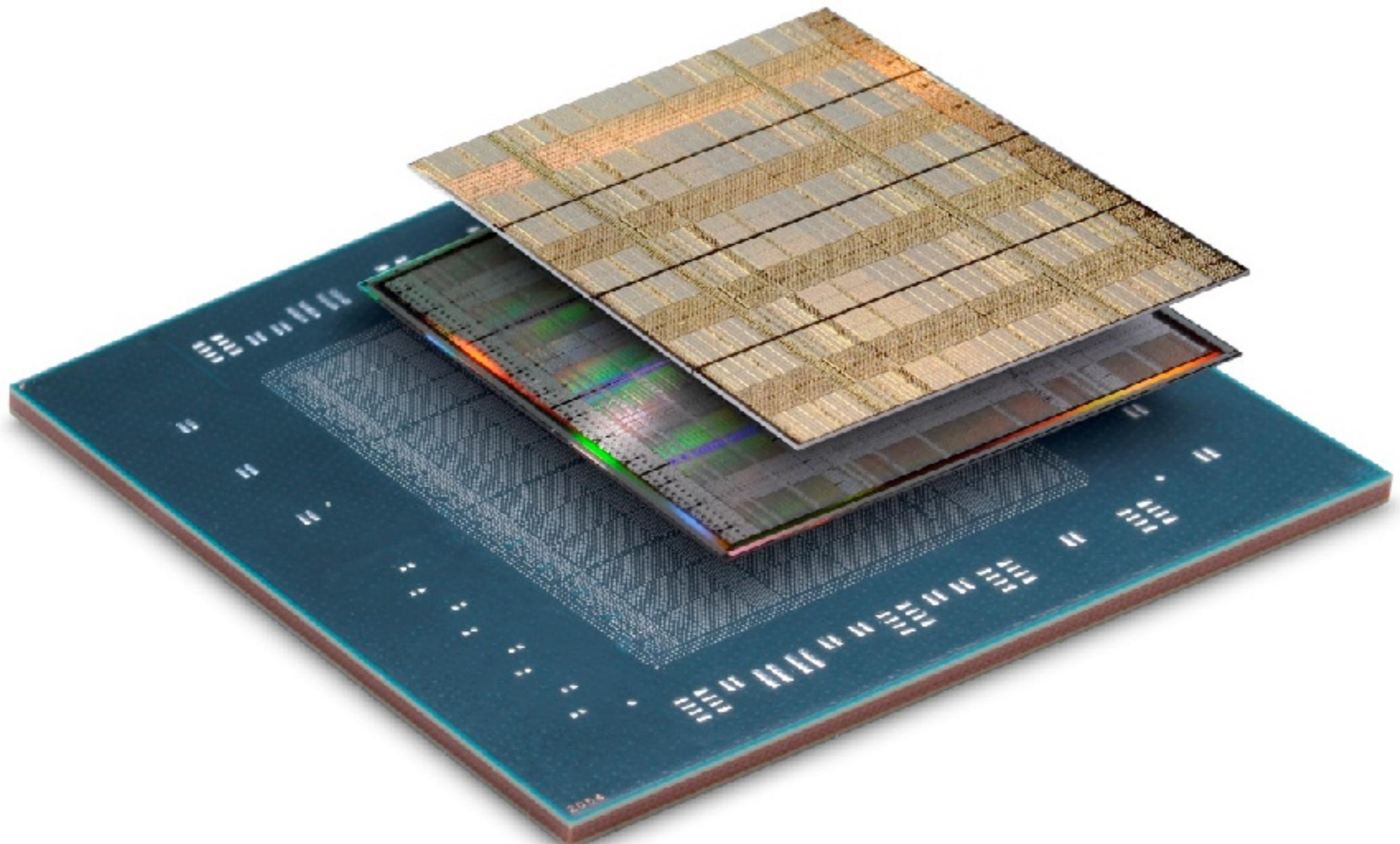

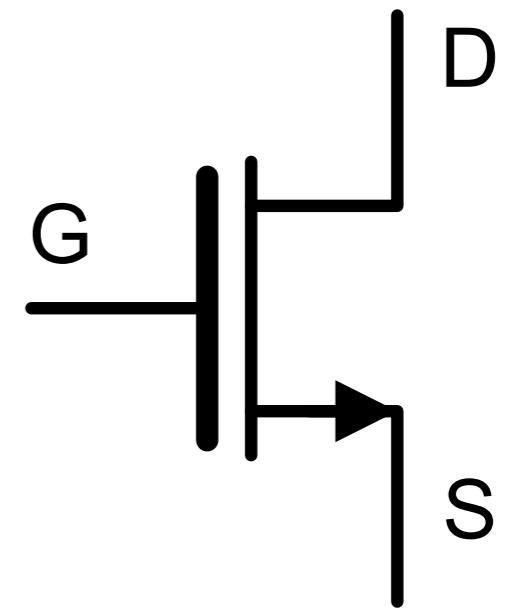6.8 Billion transistors

Transistor

- The most important device in an integrated circuit.
- An extremely complicated device
- Need computer models to describe the behavior accurately.
- [BSIM](#) model published in 1987, 17 parameters to describe a transistor. This is similar what you find in textbooks. Applies to 1um transistor lengths.



558

IEEE JOURNAL OF SOLID-STATE CIRCUITS, VOL. SC-22, NO. 4, AUGUST 1987

BSIM: Berkeley Short-Channel IGFET Model for MOS Transistors

BING J. SHEU, MEMBER, IEEE, DONALD L. SCHIARFETTER, FELLOW, IEEE, PING-KEUNG KO, MEMBER, IEEE,
AND MIN-CHIE JENG

Abstract—The Berkeley Short-channel IGFET Model (BSIM), an accurate and computationally efficient MOS transistor model, and its associated characterization facility for advanced integrated-circuit design are described. Both the strong-inversion and weak-inversion components of the drain-current expression are included. In order to speed up the circuit-simulation execution time, the dependence of the drain current on the substrate bias has been modeled with a numerical approximation. This approximation also simplifies the transistor terminal charge expressions. The charge model was derived from its drain-current counterpart to

only as accurate as the models used. In the past, the SPICE2 program has provided three built-in MOS transistor models [6]. The Level-1 model, which contains fairly simple expressions, is most suitable for preliminary analysis. The Level-2 model, which contains expressions from detailed device physics, does not work well for small-geometry transistors. The Level-3 model represents an attempt to pursue the semi-empirical model-line approach

3. *Saturation Region* [$V_{GS} > V_{th}$ and $V_{DS} \geq V_{DSAT}$]:

$$I_{DS} = \frac{\mu_0}{[1 + U_0(V_{GS} - V_{th})]} \cdot \frac{W}{L} \cdot \frac{C_{ox}}{2aK} (V_{GS} - V_{th})^2$$

BSIM 4.5 = 284 parameters

```
.MODEL N1 NMOS LEVEL=14 VERSION=4.5.0 BINUNIT=1 PARAMCHK=1 MOBMOD=0 CAPMOD=2 IGMOD=1 IGBMOD=1 GEOMOD=1  
DIOMOD=1 RDMSMOD=0 RBODYMOD=0 RGATEMOD=3 PERMOD=1 ACNQSMOD=0 TRNQSMOD=0 TEMPMOD=0 TNOM=27  
TOXE=1.8E-009 TOXP=10E-010 TOXM=1.8E-009 DTOX=8E-10 EPSROX=3.9 WINT=5E-009 LINT=1E-009 LL=0 WL=0 LLN=1 WLN=1 LW=0  
WW=0 LWN=1 WWN=1 LWL=0 WWL=0 XPART=0 TOXREF=1.4E-009 SAREF=5E-6 SBREF=5E-6 WLOD=2E-6 KU0=-4E-6 KVSAT=0.2  
KVTH0=-2E-8 TKU0=0.0 LLODKU0=1.1 WLODKU0=1.1 LLODVTH=1.0 WLODVTH=1.0 LKU0=1E-6 WKU0=1E-6 PKU0=0.0 LKVTH0=1.1E-6  
WKVTH0=1.1E-6 PKVTH0=0.0 STK2=0.0 LODK2=1.0 STETA0=0.0 LODETA0=1.0 LAMBDA=4E-10 VSAT=1.1E 005 VTL=2.0E5 XN=6.0 LC=5E-9  
RNOIA=0.577 RNOIB=0.37 LINTNOI=1E-009 WPEMOD=0 WEB=0.0 WEC=0.0 KVTH0WE=1.0 K2WE=1.0 KU0WE=1.0 SCREF=5.0E-6  
TVOFF=0.0 TVFBSDOFF=0.0 VTH0=0.25 K1=0.35 K2=0.05 K3=0 K3B=0 W0=2.5E-006 DVT0=1.8 DVT1=0.52 DVT2=-0.032 DVT0W=0  
DVT1W=0 DVT2W=0 DSUB=2 MINV=0.05 VOFFL=0 DVTP0=1E-007 DVTP1=0.05 LPE0=5.75E-008 LPEB=2.3E-010 XJ=2E-008 NGATE=5E  
020 NDEP=2.8E 018 NSD=1E 020 PHIN=0 CDSC=0.0002 CDSCB=0 CDSCD=0 CIT=0 VOFF=-0.15 NFACTOR=1.2 ETA0=0.05 ETAB=0  
UC=-3E-011 VFB=-0.55 U0=0.032 UA=5.0E-011 UB=3.5E-018 A0=2 AGS=1E-020 A1=0 A2=1 B0=-1E-020 B1=0 KETA=0.04 DWG=0 DWB=0  
PCLM=0.08 PDIBLC1=0.028 PDIBLC2=0.022 PDIBLCB=-0.005 DROUT=0.45 PVAG=1E-020 DELTA=0.01 PSCBE1=8.14E 008 PSCBE2=5E-008  
RSH=0 RDSW=0 RSW=0 RDW=0 FPROUT=0.2 PDITS=0.2 PDITSD=0.23 PDITSL=2.3E 006 RSH=0 RDSW=50 RSW=150 RDW=150  
RDSWMIN=0 RDWMIN=0 RSWMIN=0 PRWG=0 PRWB=6.8E-011 WR=1 ALPHA0=0.074 ALPHA1=0.005 BETA0=30 AGIDL=0.0002  
BGIDL=2.1E 009 CGIDL=0.0002 EGIDL=0.8 AIGBACC=0.012 BIGBACC=0.0028 CIGBACC=0.002 NIGBACC=1 AIGBINV=0.014 BIGBINV=0.004  
CIGBINV=0.004 EIGBINV=1.1 NIGBINV=3 AIGC=0.012 BIGC=0.0028 CIGC=0.002 AIGSD=0.012 BIGSD=0.0028 CIGSD=0.002 NIGC=1  
POXEDGE=1 PIGCD=1 NTOX=1 VFBSDOFF=0.0 XRCRG1=12 XRCRG2=5 CGSO=6.238E-010 CGDO=6.238E-010 CGBO=2.56E-011  
CGDL=2.495E-10 CGSL=2.495E-10 CKAPPAS=0.03 CKAPPAD=0.03 ACDE=1 MOIN=15 NOFF=0.9 VOFFCV=0.02 KT1=-0.37 KT1L=0.0  
KT2=-0.042 UTE=-1.5 UA1=1E-009 UB1=-3.5E-019 UC1=0 PRT=0 AT=53000 FNOIMOD=1 TNOIMOD=0 JSS=0.0001 JSWS=1E-011  
JSWGS=1E-010 NJS=1 IJTHSFWD=0.01 IJTHSREV=0.001 BVS=10 XJBVS=1 JSD=0.0001 JSWD=1E-011 JSWGD=1E-010 NJD=1  
IJTHDFWD=0.01 IJTHDREV=0.001 BVD=10 XJBVD=1 PBS=1 CJS=0.0005 MJS=0.5 PBSWS=1 CJSWS=5E-010 MJSWS=0.33 PBSWGS=1  
CJSWGS=3E-010 MJSWGS=0.33 PBD=1 CJD=0.0005 MJD=0.5 PBSWD=1 CJSWD=5E-010 MJSWD=0.33 PBSWGD=1 CJSWGD=5E-010  
MJSWGD=0.33 TPB=0.005 TCJ=0.001 TPBSW=0.005 TCJSW=0.001 TPBSWG=0.005 TCJSWG=0.001 XTIS=3 XTID=3 DMCG=0E-006  
DMCI=0E-006 DMDG=0E-006 DMCGT=0E-007 DWJ=0.0E-008 XGW=0E-007 XGL=0E-008 RSHG=0.4 GBMIN=1E-010 RBPB=5 RBPD=15  
RBPS=15 RBDB=15 RBSB=15 NGCON=1 JTSS=1E-4 JTSD=1E-4 JTSSWS=1E-10 JTSSWD=1E-10 JTSSWGS=1E-7 JTSSWGD=1E-7 NJTS=20.0  
NJTSSW=20 NJTSSWG=6 VTSS=10 VTSD=10 VTSSWS=10 VTSSWD=10 VTSSWGS=2 VTSSWGD=2 XTSS=0.02 XTSD=0.02 XTSSWS=0.02  
XTSSWD=0.02 XTSSWGS=0.02 XTSSWGD=0.02
```

BSIM 4.7 table of contents

Chapter 1: Effective Oxide Thickness, Channel Length and Channel Width	5.7.1 Channel Length Modulation (CLM)	9.1 Charge-Deficit Non-Quasi-Static (NQS) Model.....	Chapter 13: Temperature Dependence Model
1.1 Gate Dielectric Model.....	5.7.2 Drain-Induced Barrier Lowering (DIBL).....	9.1.1 Transient Model	13.1 Temperature Dependence of Threshold
1.2 Poly-Silicon Gate Depletion.....	5.7.3 Substrate Current Induced Body Effect (SCBE)	9.1.2 AC Model	13.2 Temperature Dependence of Mobility
Chapter 2: Threshold Voltage Model	5.7.4 Drain-Induced Threshold Shift (DITS) by Pocket Implant	9.2 Gate Electrode Electrode and Intrinsic-Input Resistance (IIR) Model	13.3 Temperature Dependence of Saturation Velocity
2.1 Long-Channel Model With Uniform Doping.....	5.8 Single-Equation Channel Current Model.....	9.2.1 General Description.....	13.4 Temperature Dependence of LDD.....
2.2 Non-Uniform Vertical Doping.....	5.9 New Current Saturation Mechanisms: Velocity Overshoot and ! Model	9.2.2 Model Option and Schematic.....	13.5 Temperature Dependence of Junction
2.3 Non-Uniform Lateral Doping: Pocket (Halo) Implant	5.9.1 Velocity Overshoot	9.3 Substrate Resistance Network	13.6 Temperature Dependence of Junction Diode CV
2.4 Short-Channel and DIBL Effects.....	5.9.2 Source End Velocity Limit Model.....	9.3.1 General Description.....	13.7 Temperature Dependences of E_g and n
2.5 Narrow-Width Effect	Chapter 6: Body Current Models.....	9.3.2 Model Selector and Topology.....	Chapter 14: Stress Effect Model
Chapter 3: Channel Charge and Subthreshold Swing Models.....	6.1 I_b Model	Chapter 10: Noise Modeling.....	14.1 Stress Effect Model Development
3.1 Channel Charge Model	6.2 I_{GD} and I_{GS} Model	10.1 Flicker Noise Models	14.1.1 Mobility-related Equations
3.2 Subthreshold Swing n	Chapter 7: Capacitance Model	10.1.1 General Description	14.1.2 V _{th} -related Equations
Chapter 4: Gate Direct Tunneling Current Model	7.1 General Description	10.1.2 Equations	14.1.3 Multiple Finger Device
4.1 Model Selectors	7.2 Methodology for Intrinsic Capacitance Modeling	10.2 Channel Thermal Noise	14.2 Effective SA and SB for Irregular LOD
4.2 Voltage Across Oxide V_{ox}	7.2.1 Basic Formulation	10.3 Other Noise Sources Modeled	Chapter 15: Well Proximity Effect Model
4.3 Equations for Tunneling Currents	7.2.2 Short Channel Model	Chapter 11: Asymmetric MOS Junction Diode Models	15.1 Well Proximity Effect Model
4.3.1 Gate-to-Substrate Current ($I_{gs} = I_{gbecc} + I_{gbev}$)	7.2.3 Single Equation Formulation	11.1 Junction Diode IV Model	
4.3.2 Gate-to-Channel Current (I_{gs}) and Gate-to-S/D (I_{gs} and I_{gd})	7.2.4 Charge partitioning	11.1.1 Source/Body Junction Diode	
4.3.3. Partition of I_{gs}	7.3 Charge-Thickness Capacitance Model (CTM)	11.1.2 Drain/Body Junction Diode	
Chapter 5: Drain Current Model	7.4 Intrinsic Capacitance Model Equations	11.1.3 Total Junction Source/Drain Diode Including Tunneling	
5.1 Bulk Charge Effect	7.4.1 capMod = 0	11.2 Junction Diode CV Model	
5.2 Unified Mobility Model	7.4.2 capMod = 1	11.2.1 Source/Body Junction Diode	
5.3 Asymmetric and Bias-Dependent Source/ Drain Resistance Model	7.5 Fringing/Overlap Capacitance Models	11.2.2 Drain/Body Junction Diode	
5.4 Drain Current for Triode Region	7.5.1 Fringing capacitance model	Chapter 12: Layout-Dependent Parasitics Models	
5.5 Velocity Saturation	7.5.2 Overlap capacitance model	12.1 Geometry Definition	
5.6 Saturation Voltage V_{dsat}	Chapter 8: New Material Models	12.2 Model Formulation and Options	
5.6.1 Intrinsic case	8.1 Model Selector	12.2.1 Effective Junction Perimeter and Area	
5.6.2 Extrinsic Case	8.2 Non-Silicon Channel	12.2.2 Source/Drain Diffusion Resistance	
5.6.3 V_{dsat} Formulation	8.3 Non-SiO ₂ Gate insulator	12.2.3 Gate Electrode Resistance	
5.7 Saturation-Region Output Conductance Model	8.4 Non-Poly Silicon Gate Dielectric	12.2.4 Option for Source/Drain Connections	
	Chapter 9: High-Speed/RF Models	12.2.5 Option for Source/Drain Contacts	

Lesson 1


It's not practical to do accurate hand calculation for transistors. Finding where to start will have to do

The story

The story




techcrunch.com

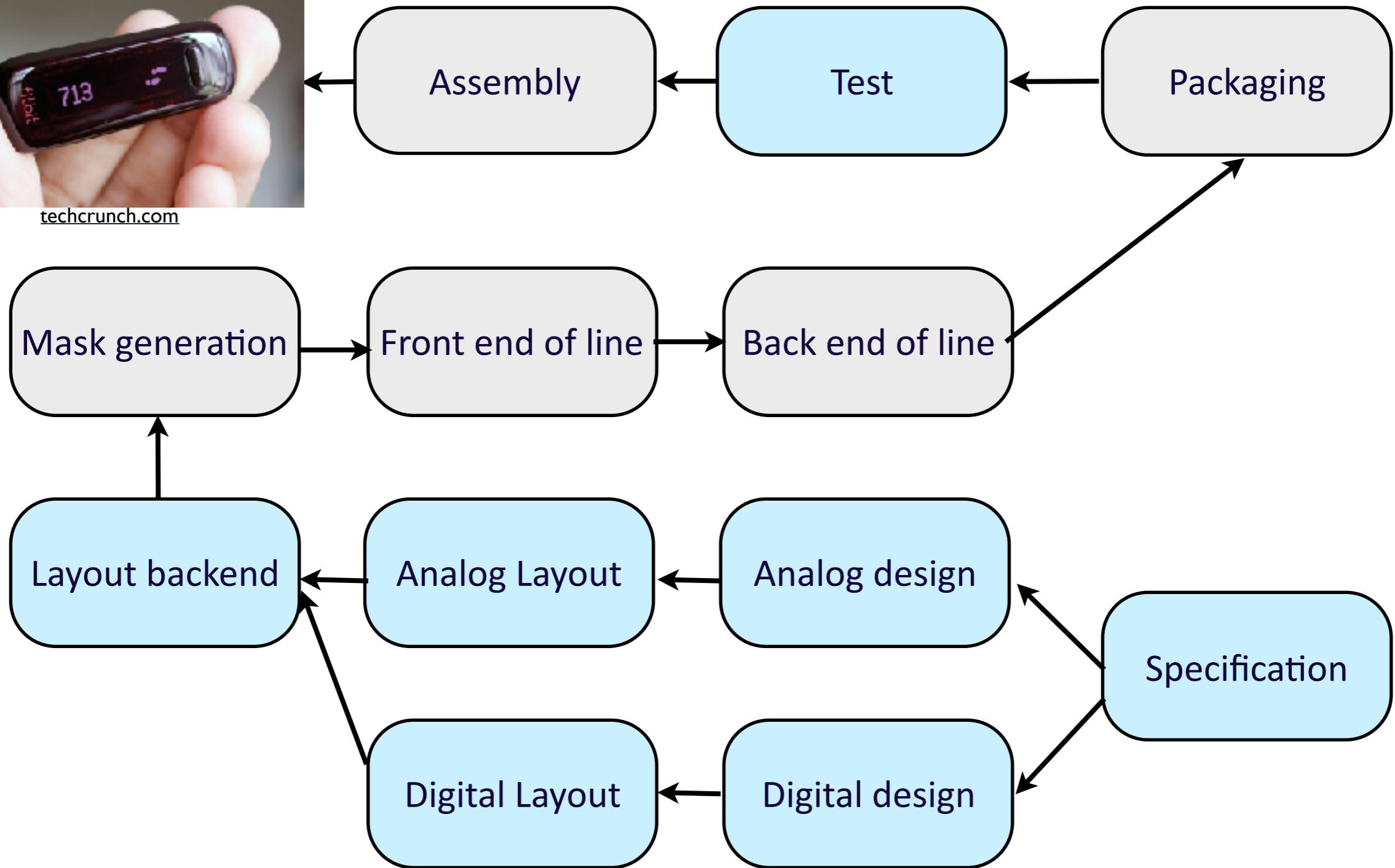

The story



techcrunch.com

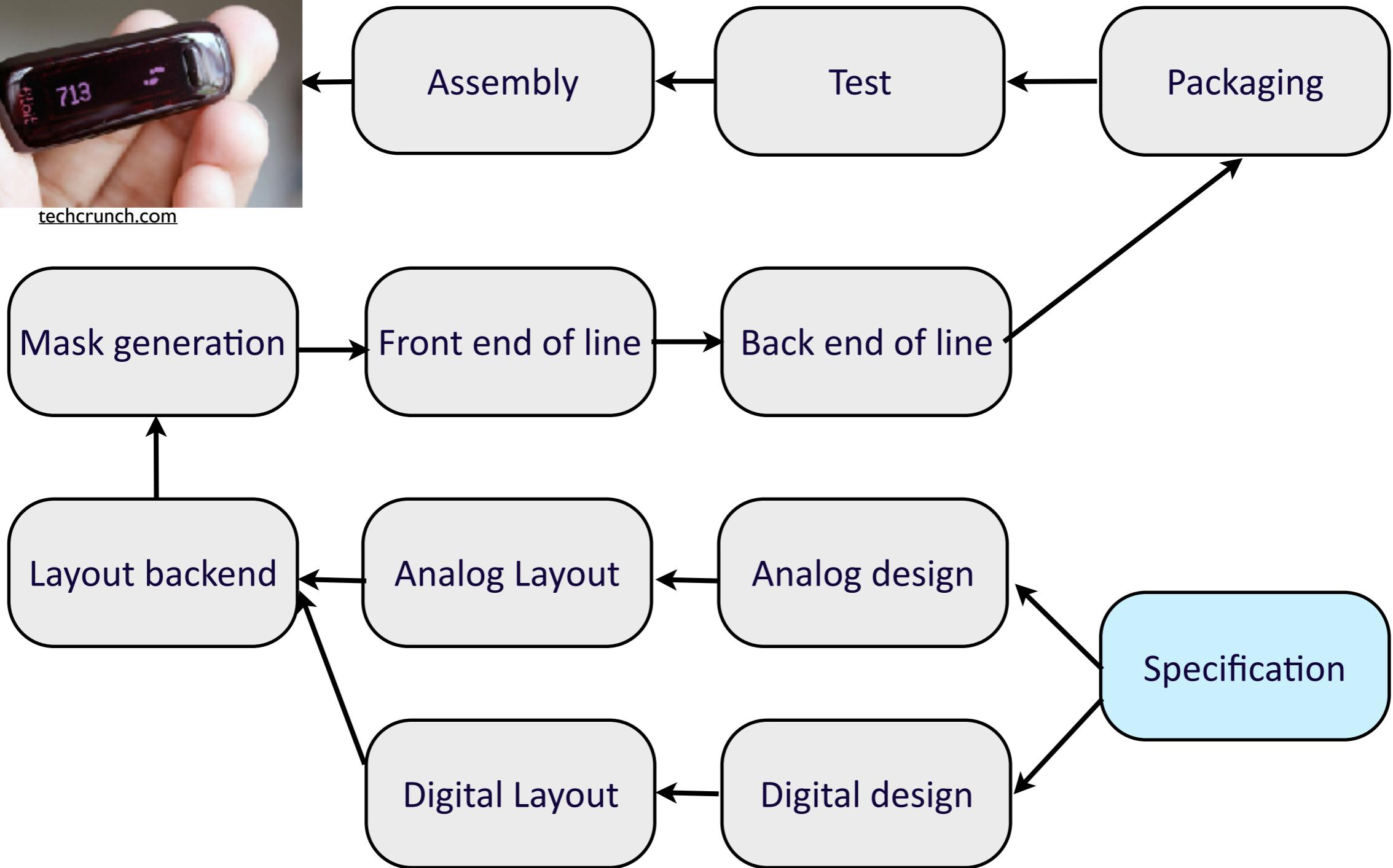

Specification

The guessing game


Specification

- Trying to figure out what we need to make
- Maybe the most difficult step in the process, because were trying to guess what customers need 2-3 years before they need it.
- Usually done by the senior designers

The story



techcrunch.com

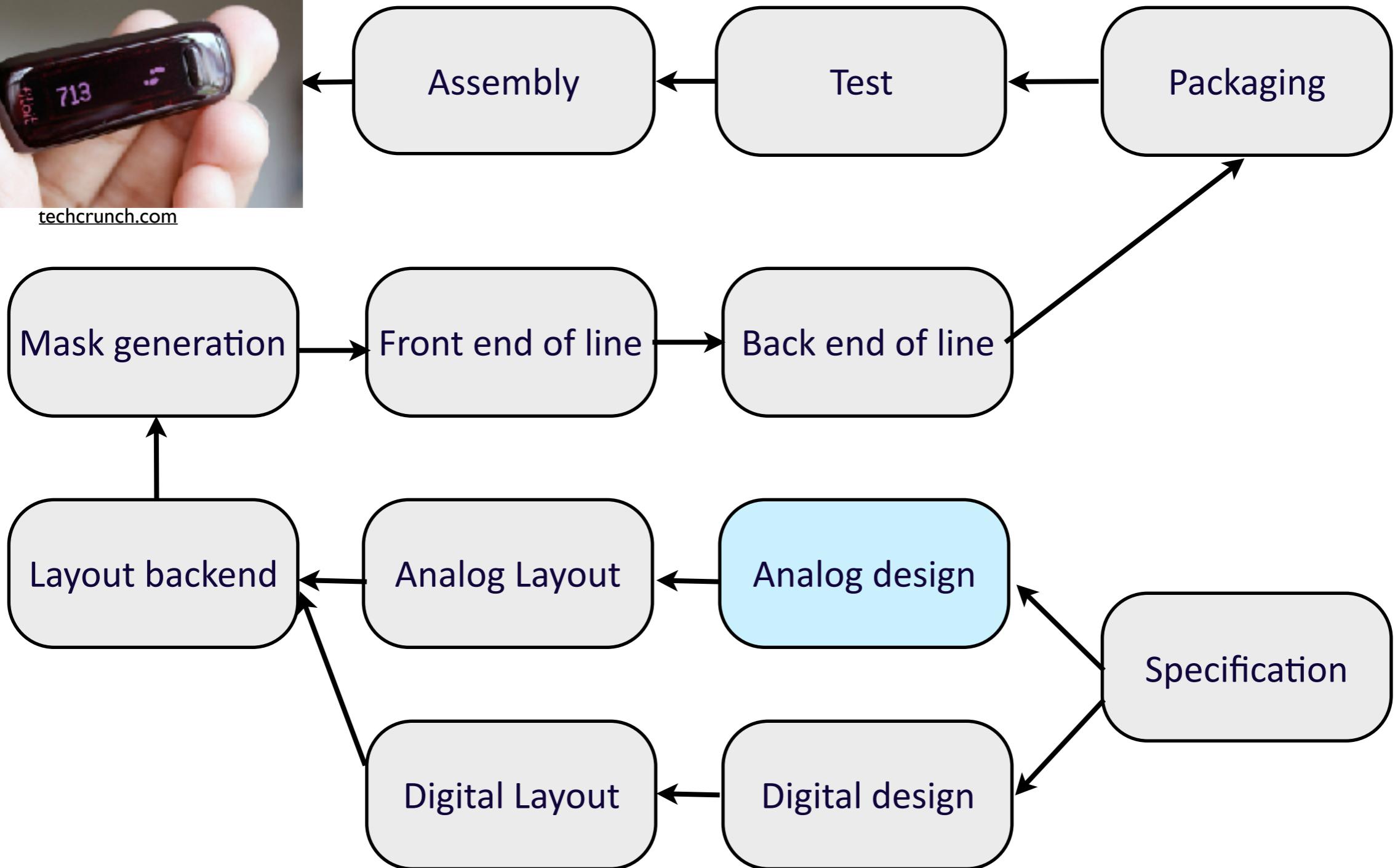

Design

The creative phase


Demo: Design of an operational transconductance amplifier

- Make an initial design of a voltage buffer of $V_{DD}/2$
- Supply: 1.2V
- Capacitive Load: 1pF
- Speed : 0.1% error after 100ns
- Current consumption: around 30uA

Transistor design tips


- NMOS $\sim 2\mu\text{A} - 10 \mu\text{A}$ per square. For example
 $W=20F$ $L=2F \sim 100\mu\text{A}$ ($F = \text{minimum gate length}$)
- PMOS $\sim 0.5\mu\text{A} - 3\mu\text{A}$ per square
- Width $\sim 1 - 20$ times the lengths

Differential OTA with CT CMFB

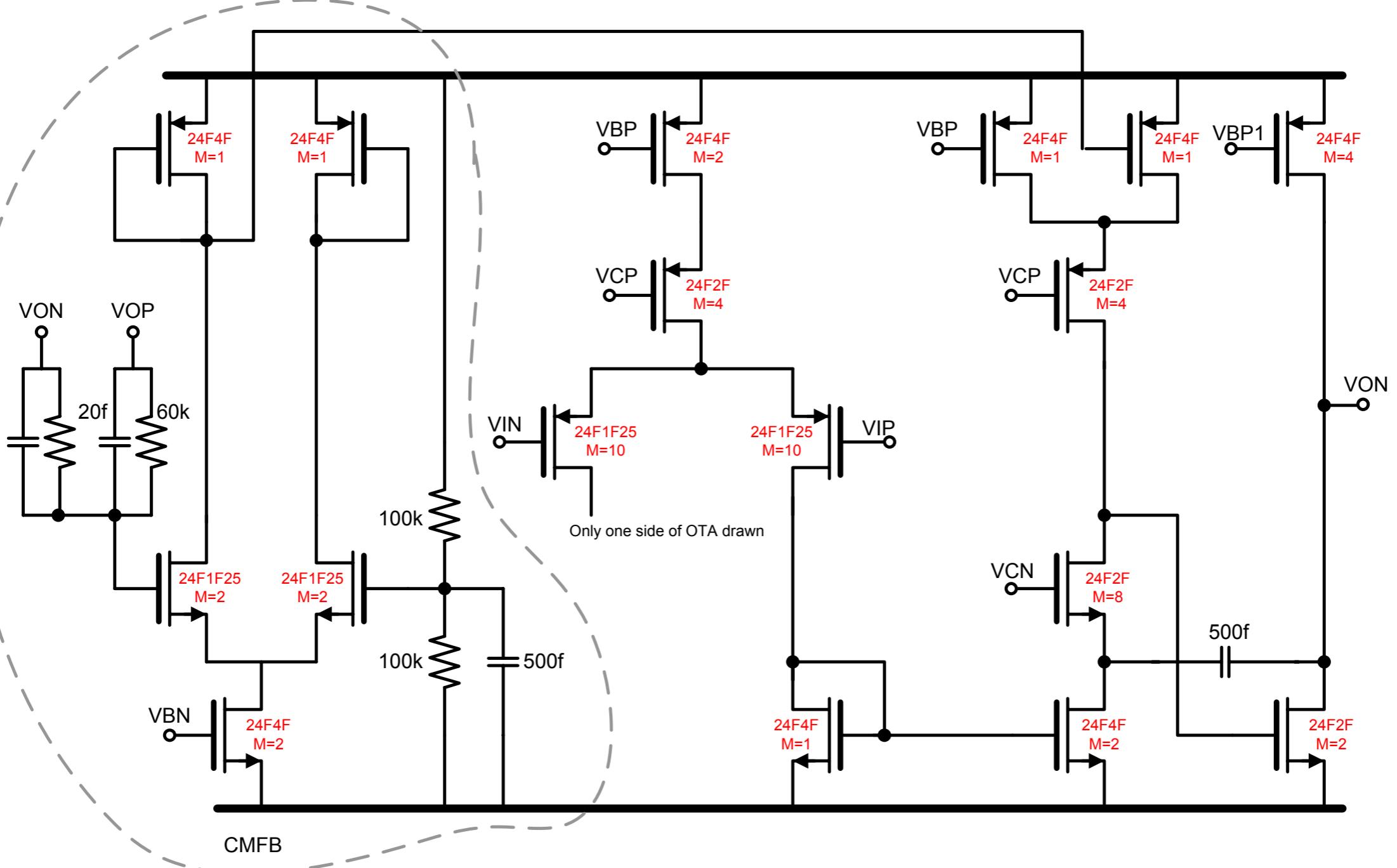


F = minimum transistor gate length. For example 24F4F => W = 24 x min gate, L= 4 x min gate


Differential OTA - Bias circuit

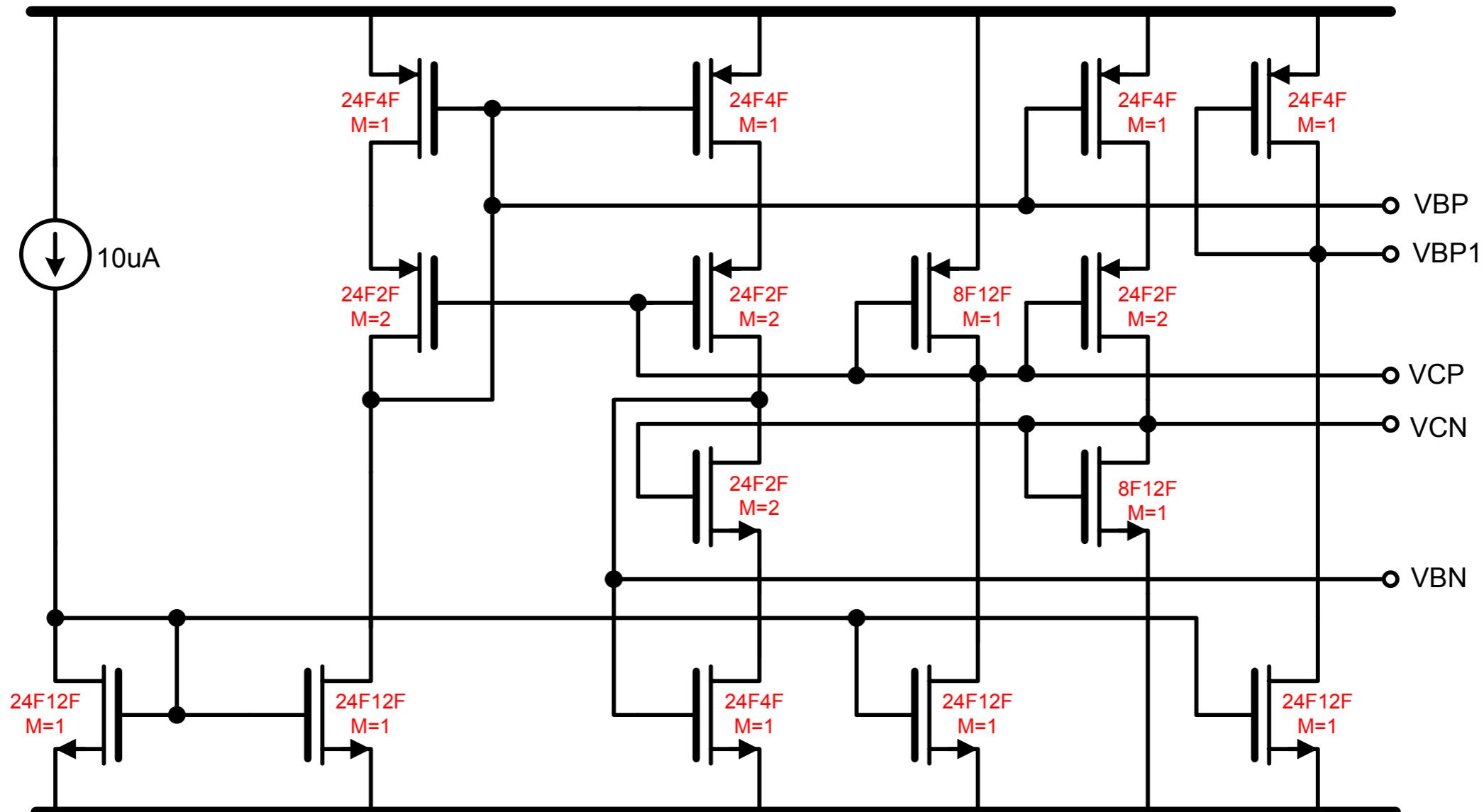

Voltage divider

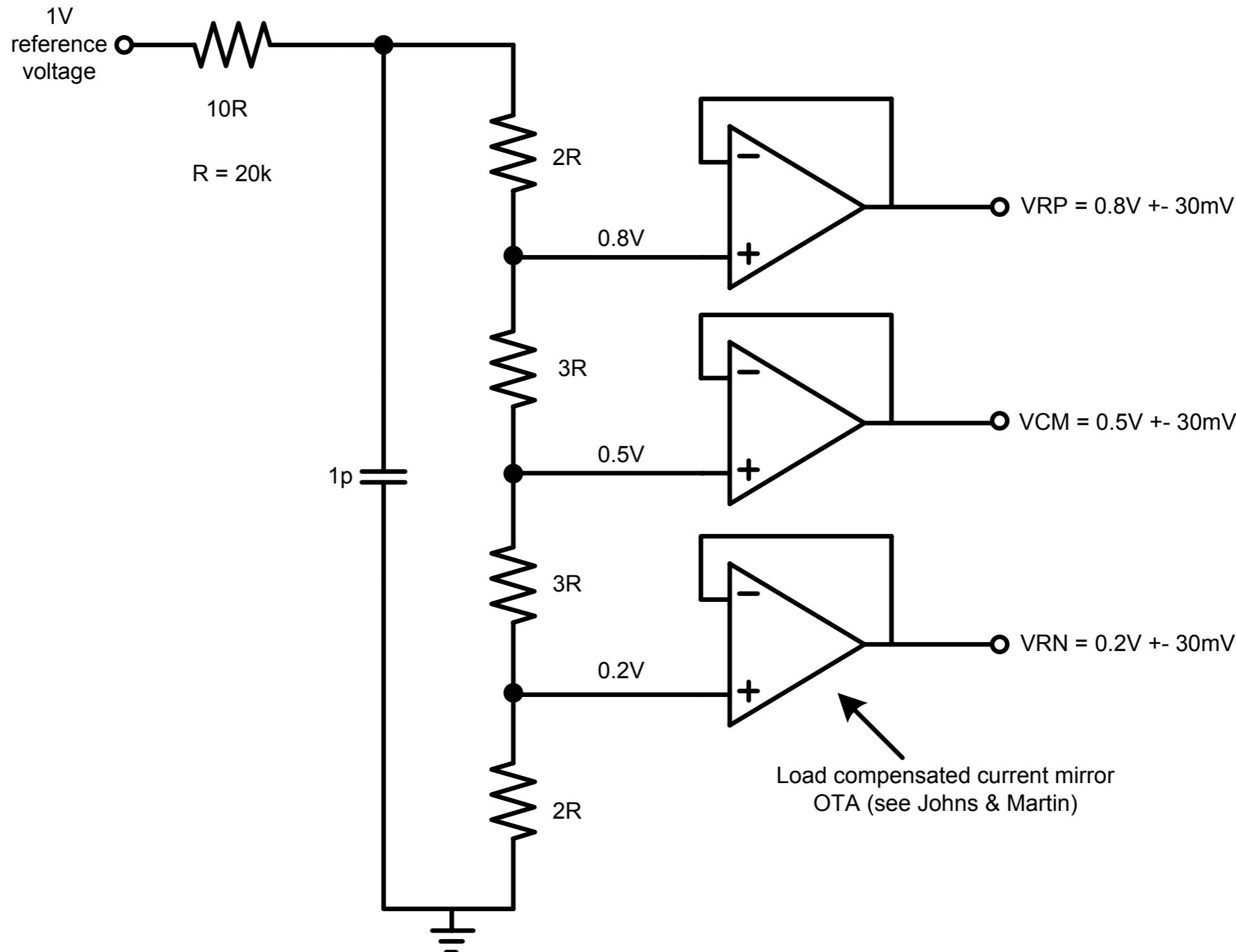

Schematic

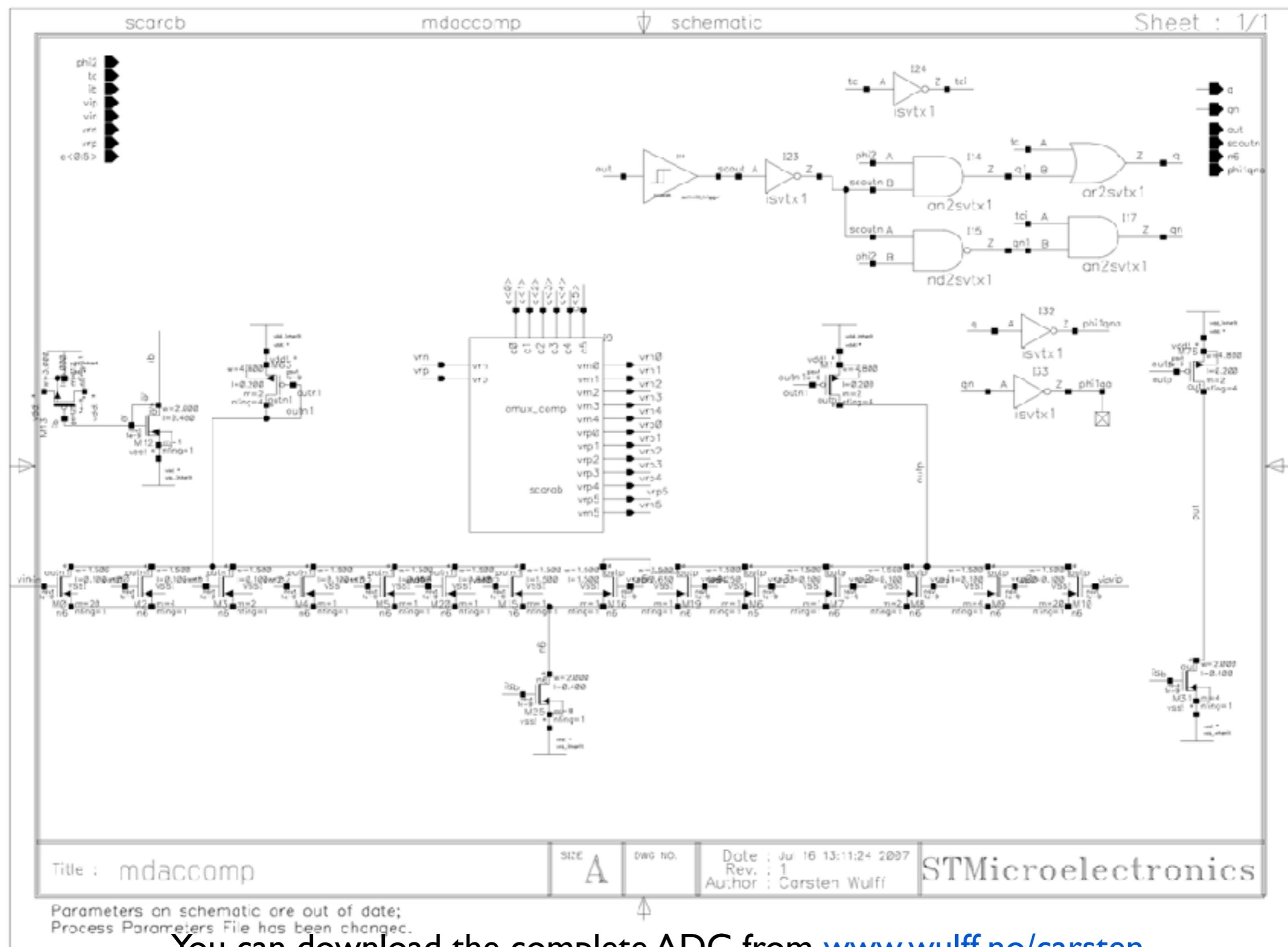


Netlist

The story



techcrunch.com

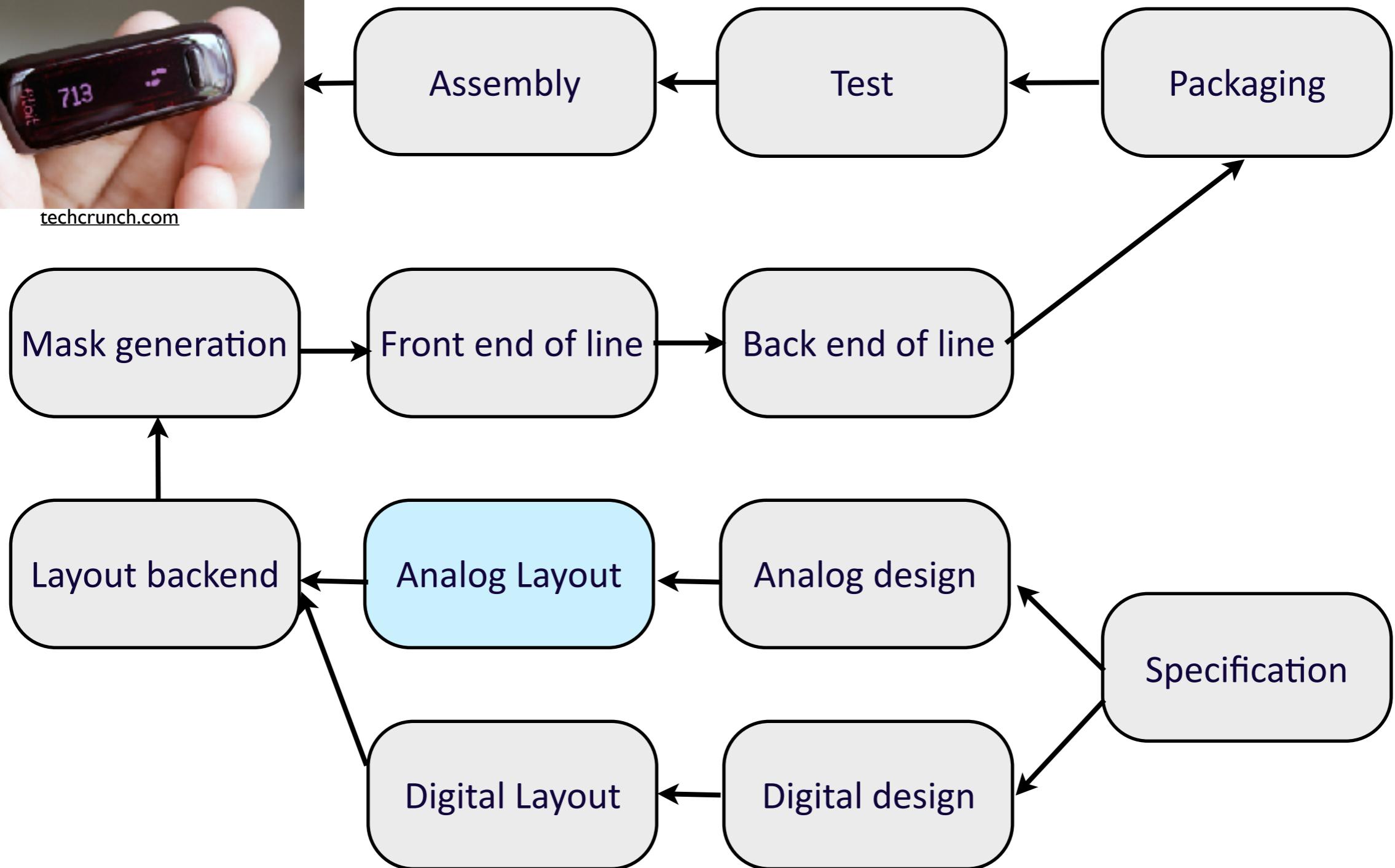

Layout


Making a GDSII file that can be sent to the foundry

Transistor layout - Diffusion




Marks the boundary of a transistor


Transistor layout - Gate

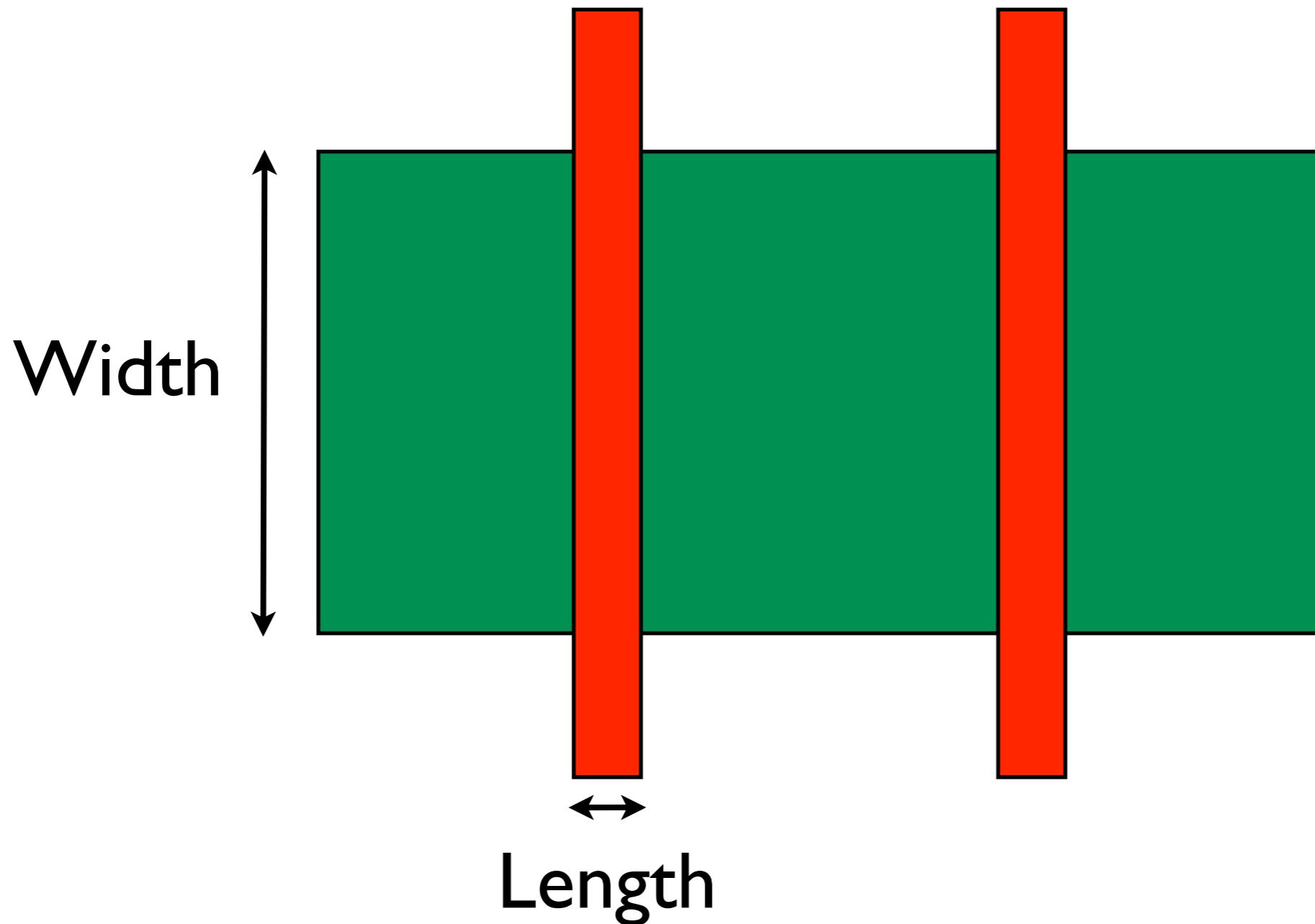


Transistor layout - Contacts

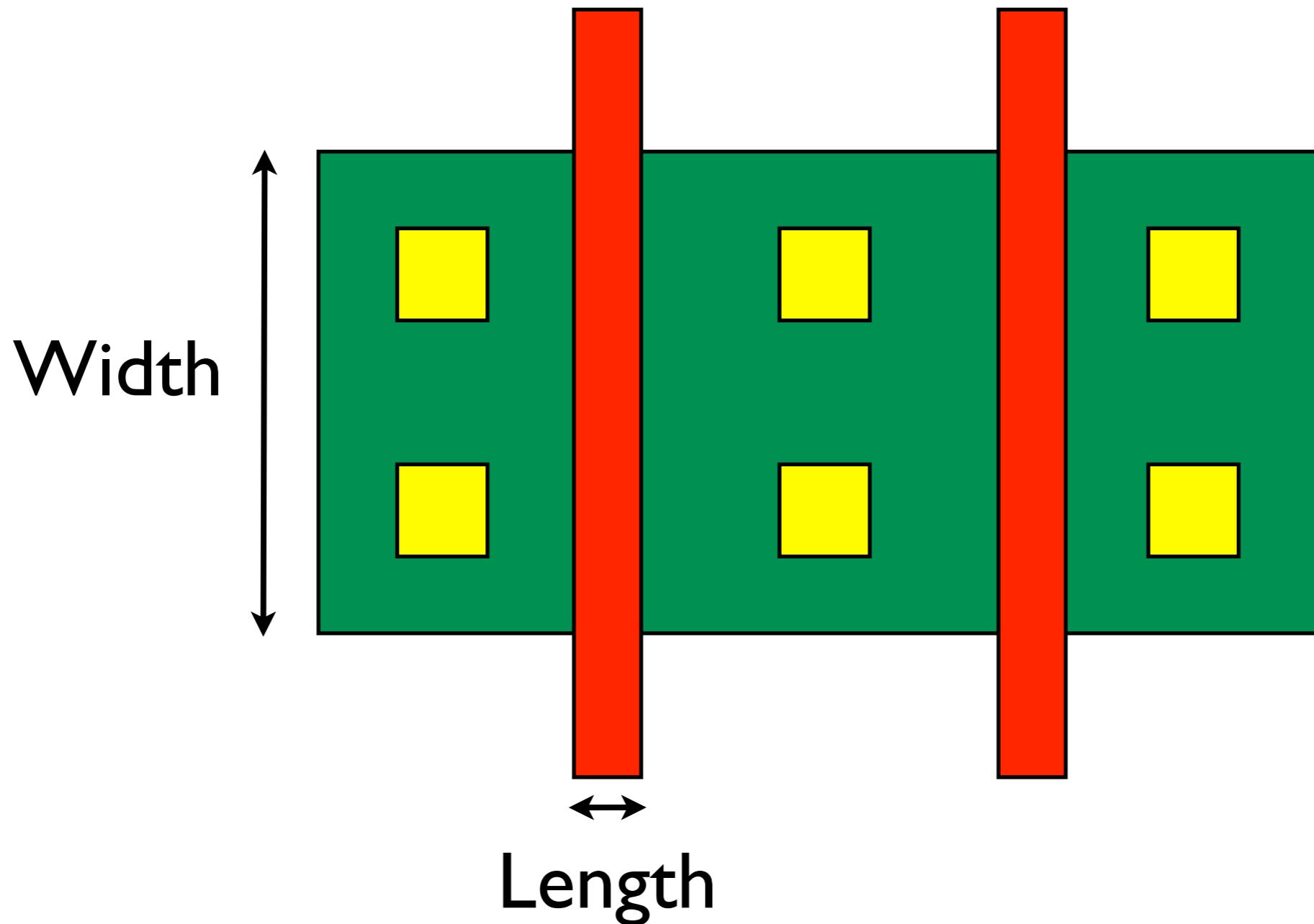

Transistor layout - Metal 1

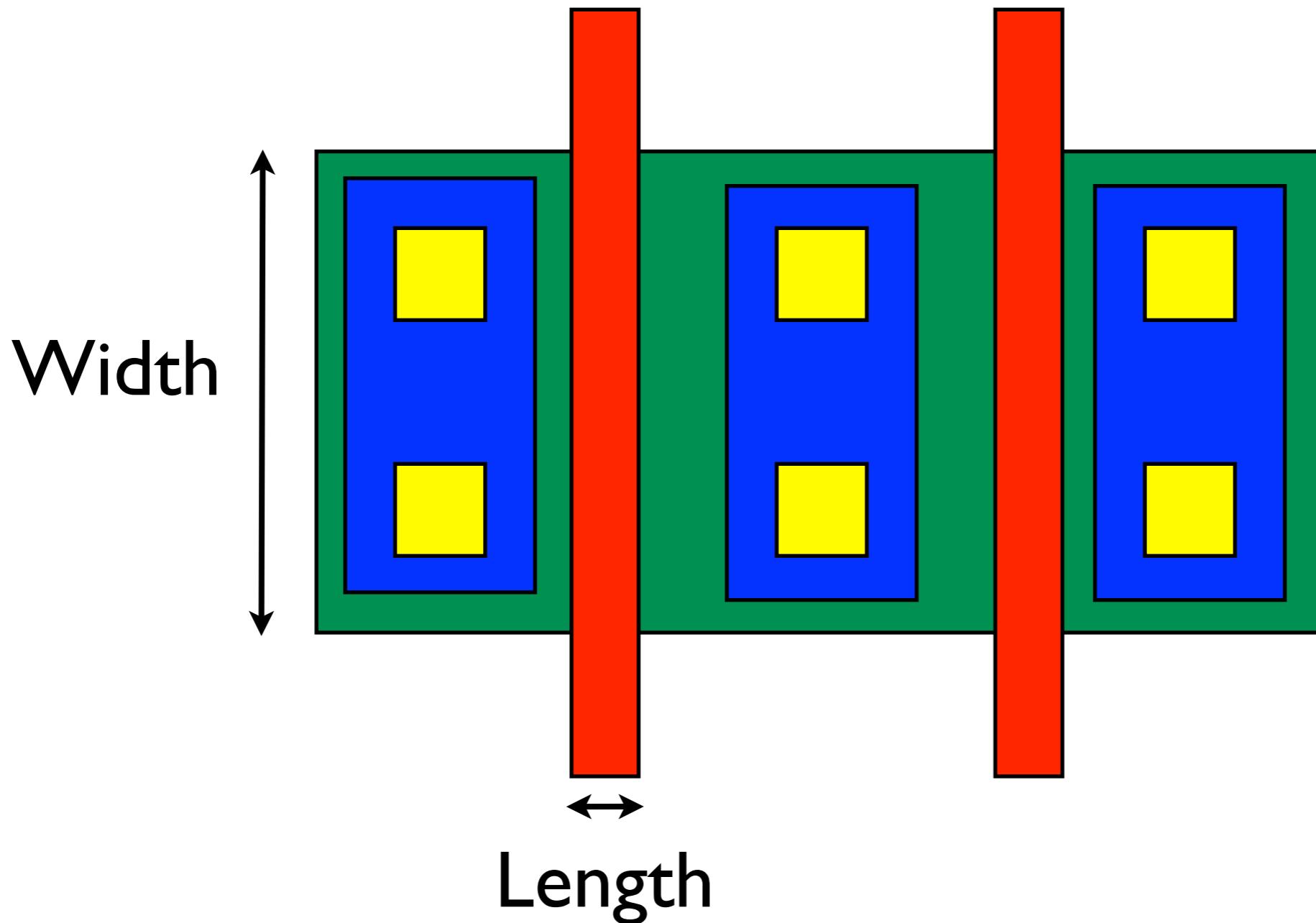

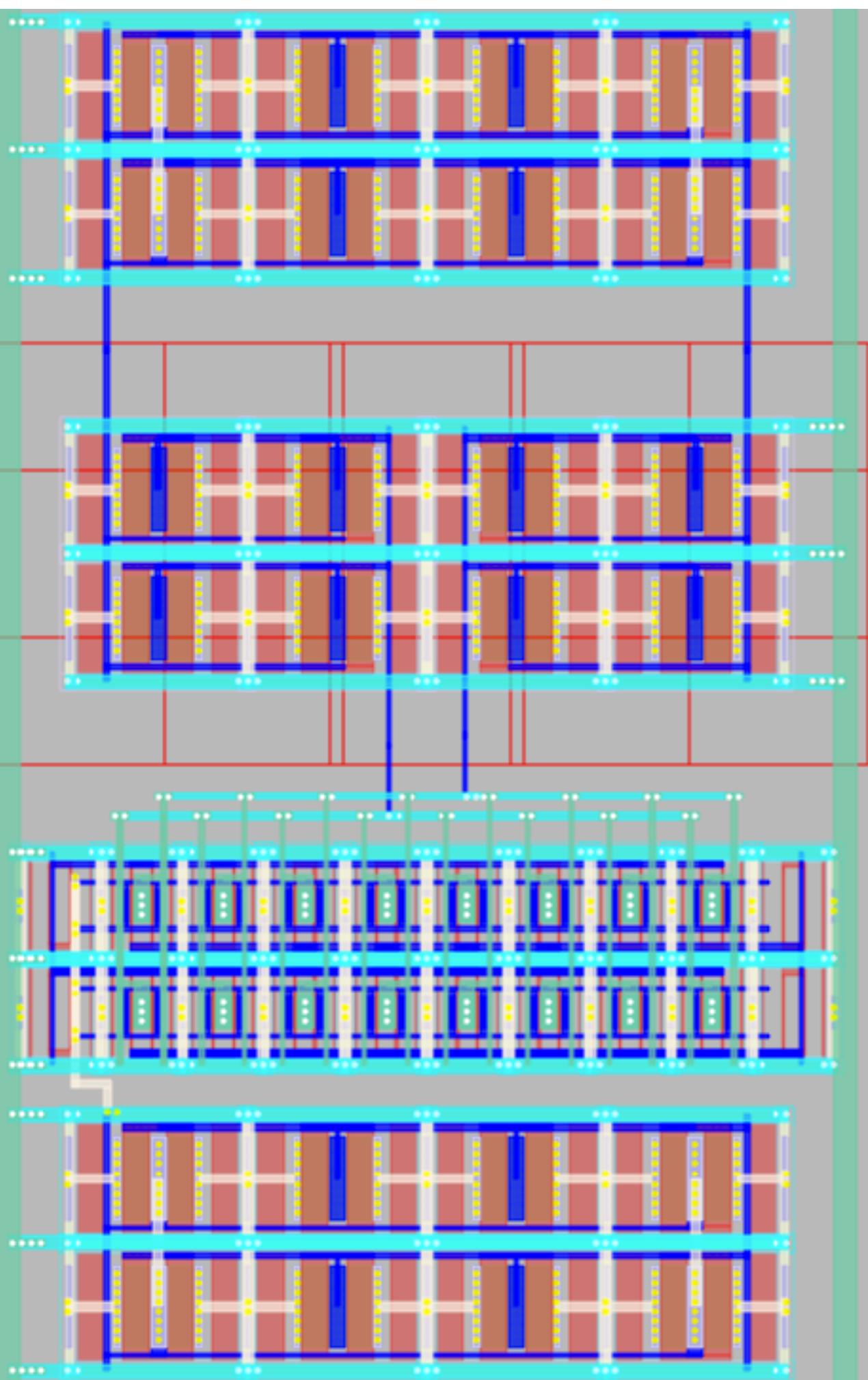Current mirror operational transconductance amplifier



Red = Poly silicon

Yellow = contacts/via

Blue = Metal I

Yellow = Metal 2


Turquoise = Metal 3

Green = Metal 4

The story




techcrunch.com

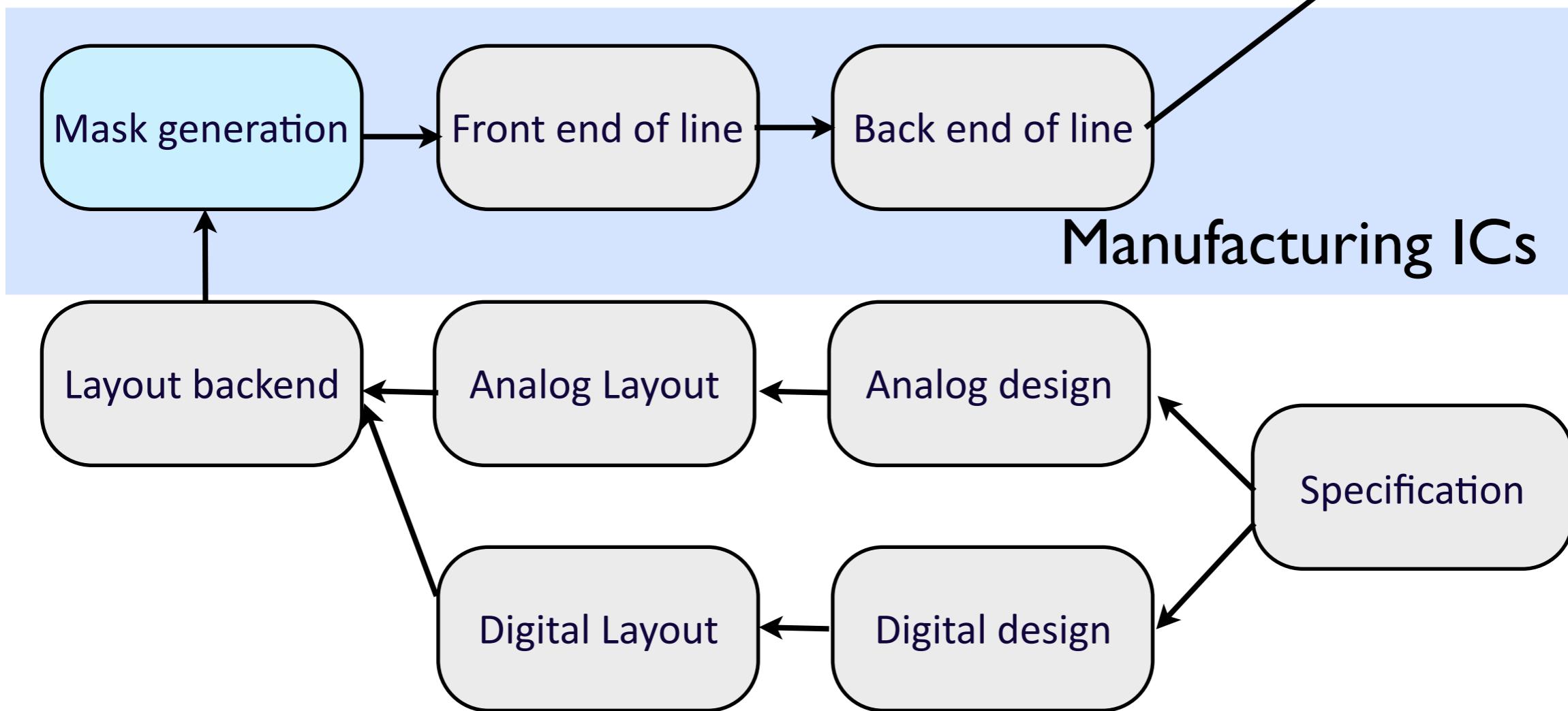

Manufacturing ICs


Extremely expensive

Mask making

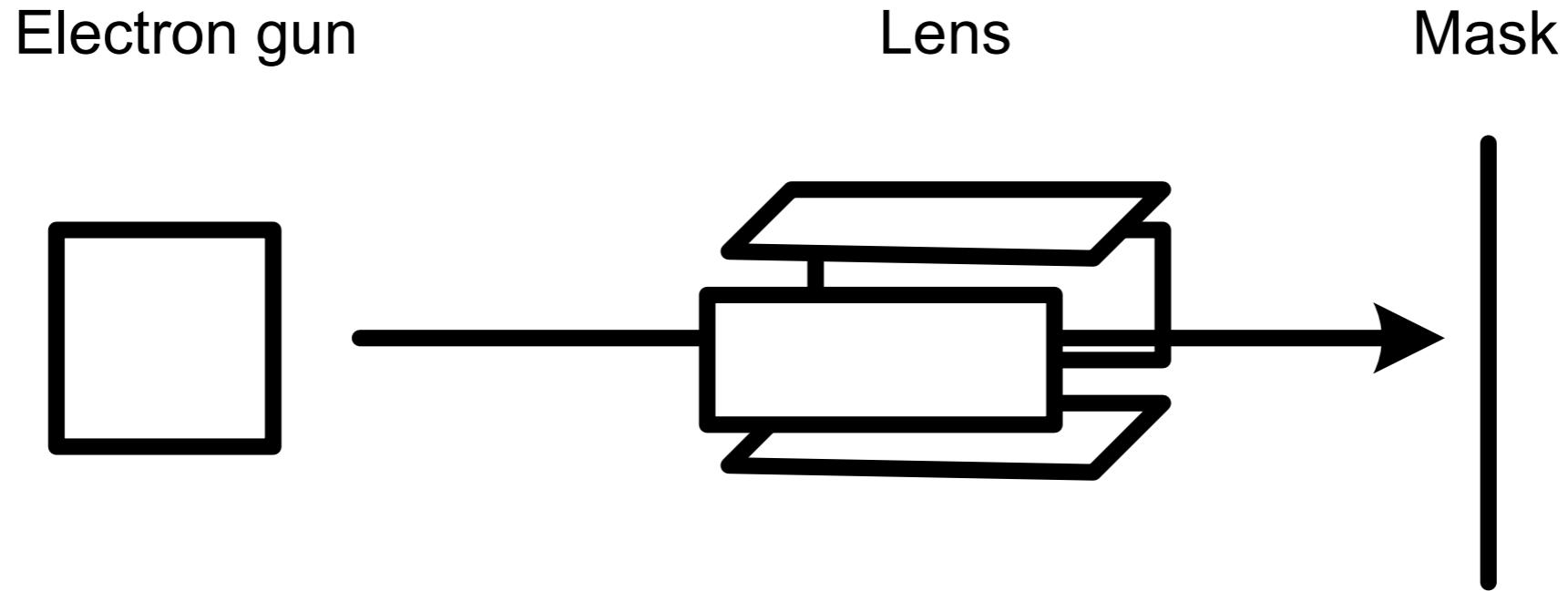

- Mask making is extremely expensive
- A normal chip has around 30 - 40 masks.

Lithography

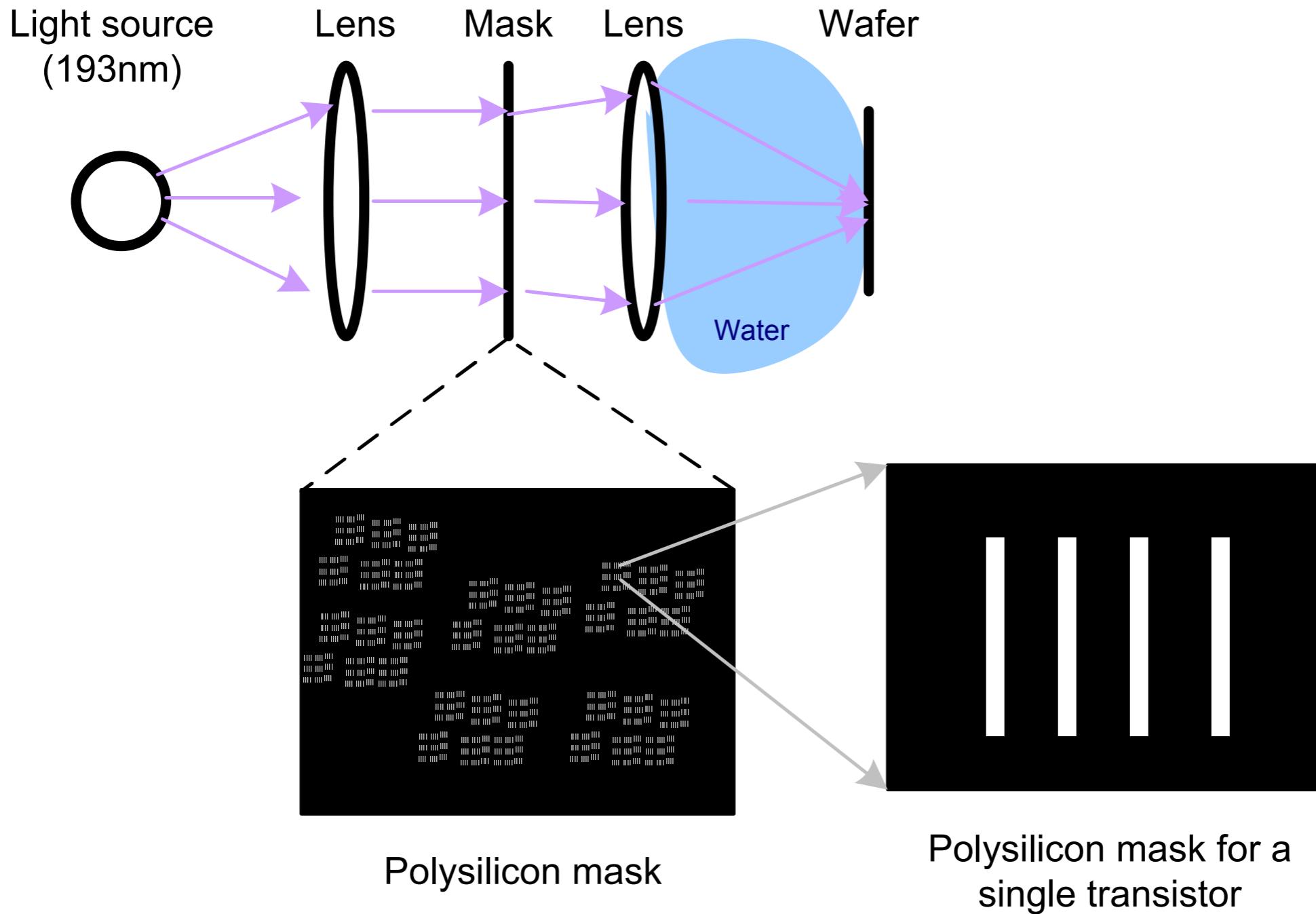

Lithography machines

Today: 193nm argon fluoride excimer laser


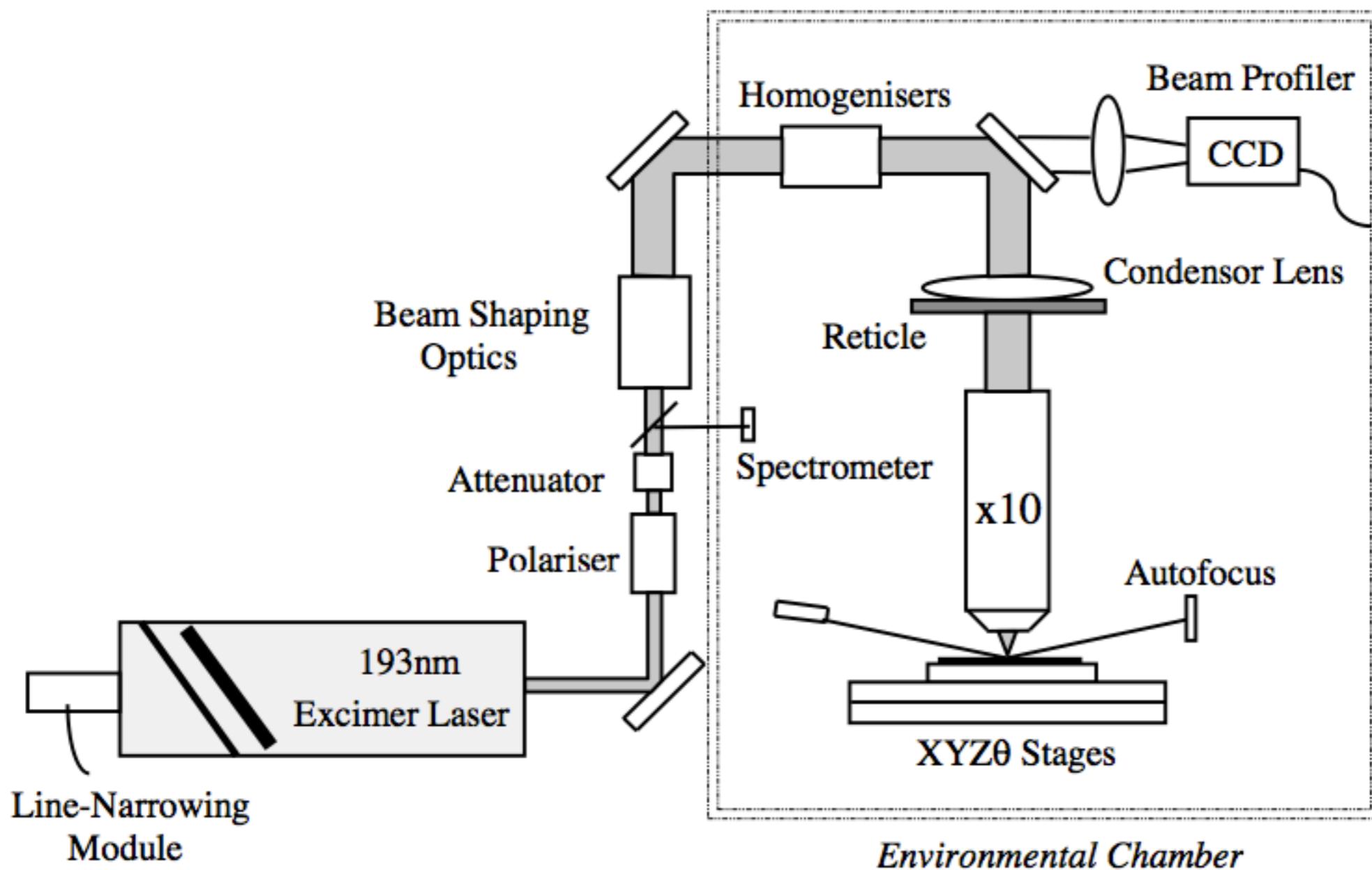


Figure 2. Schematic diagram of 193nm Microstepper

Optical proximity correction

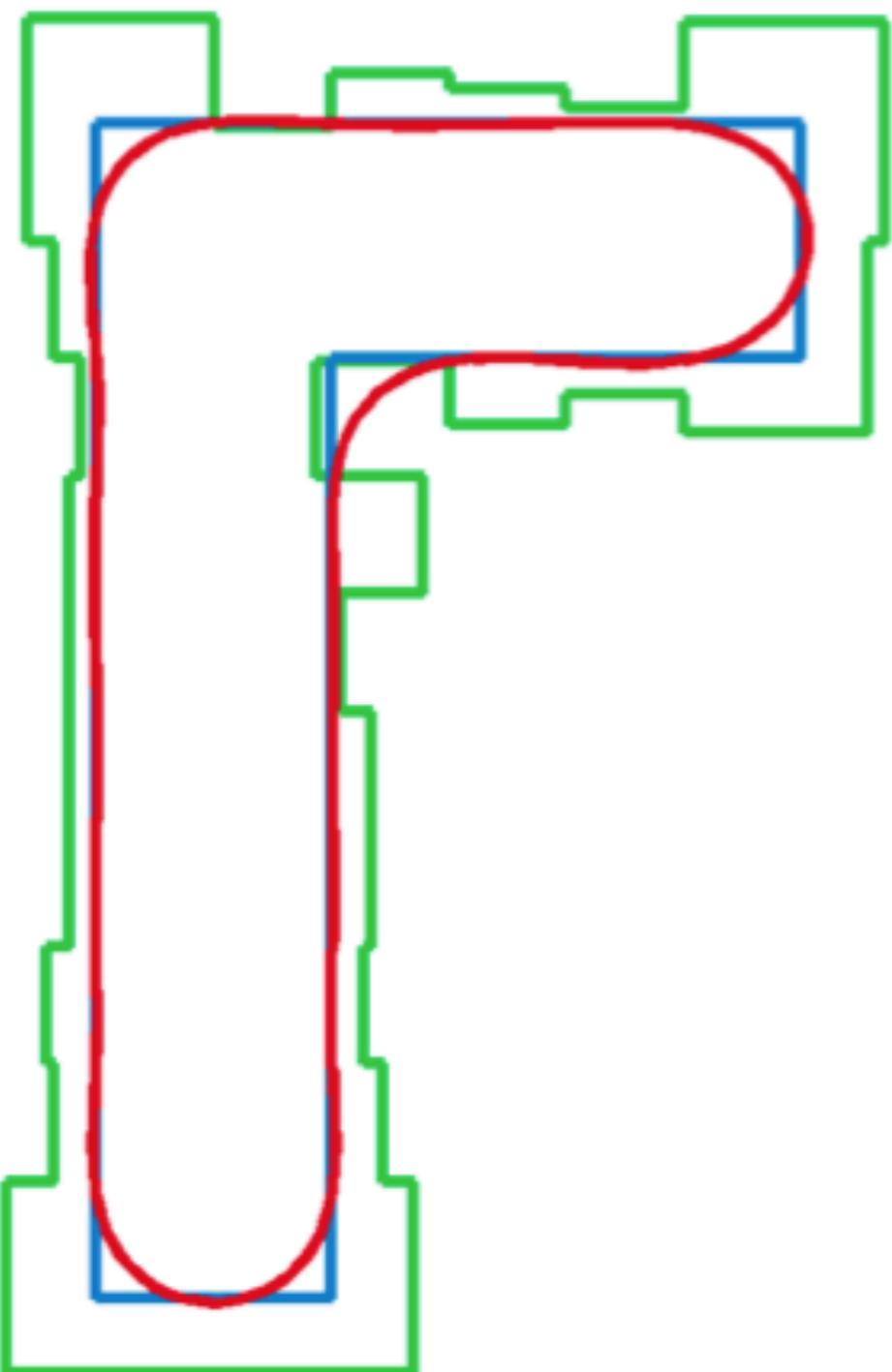


- The wavelength of the developing light is larger than minimum features ($193\text{nm} > 20\text{nm}$)
- Diffraction patterns affect the light intensity on the photo-resist
- Extensive calculations need to calculate how the mask should look to compensate for diffraction and processing inaccuracies

Blue = Pattern we draw in our CAD programs

Green = How the mask actually looks

Red = Pattern on chip

Tomorrow (maybe): Extreme ultra violet

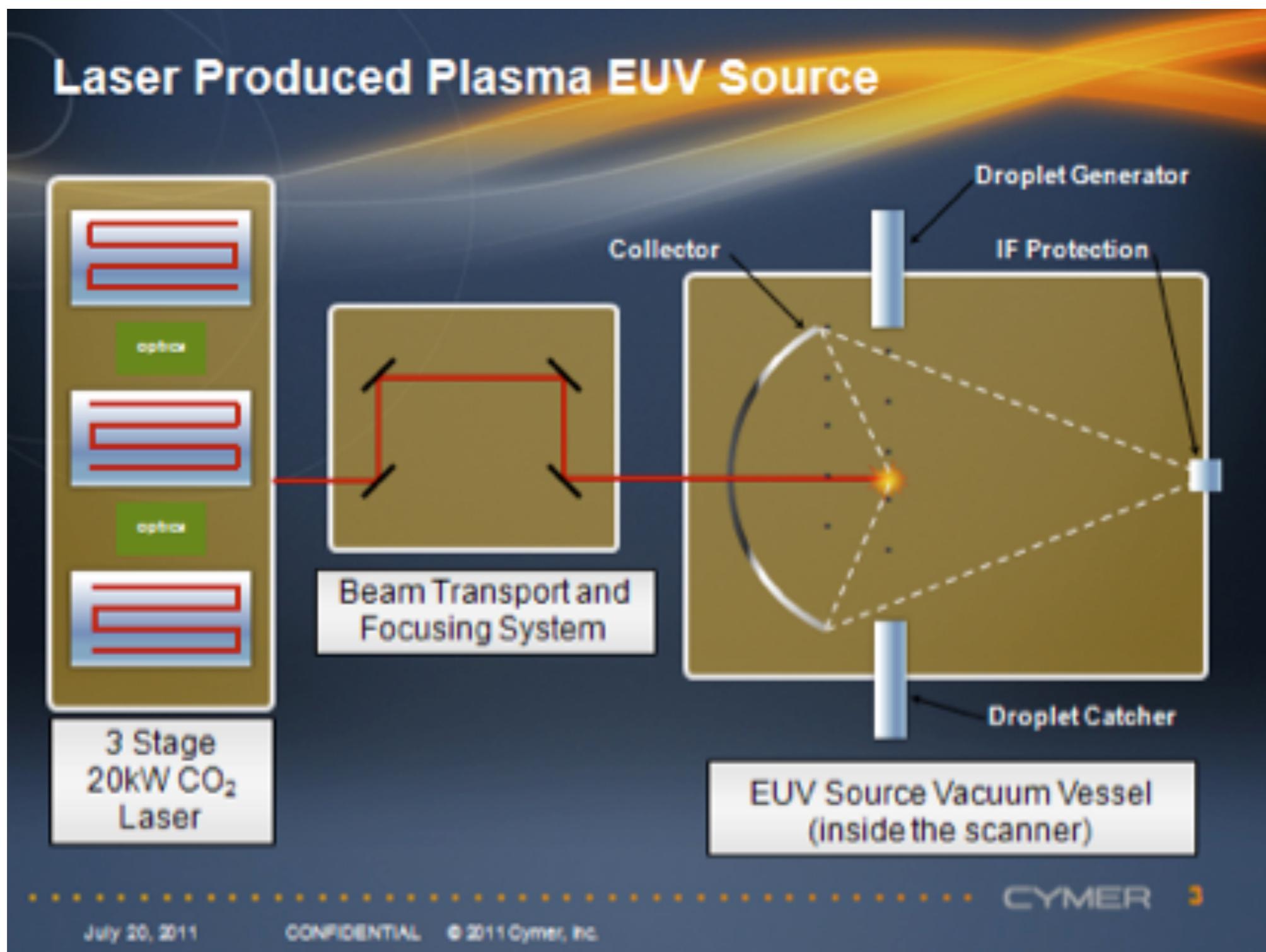


“At least another decade”: What Next?


The story




techcrunch.com

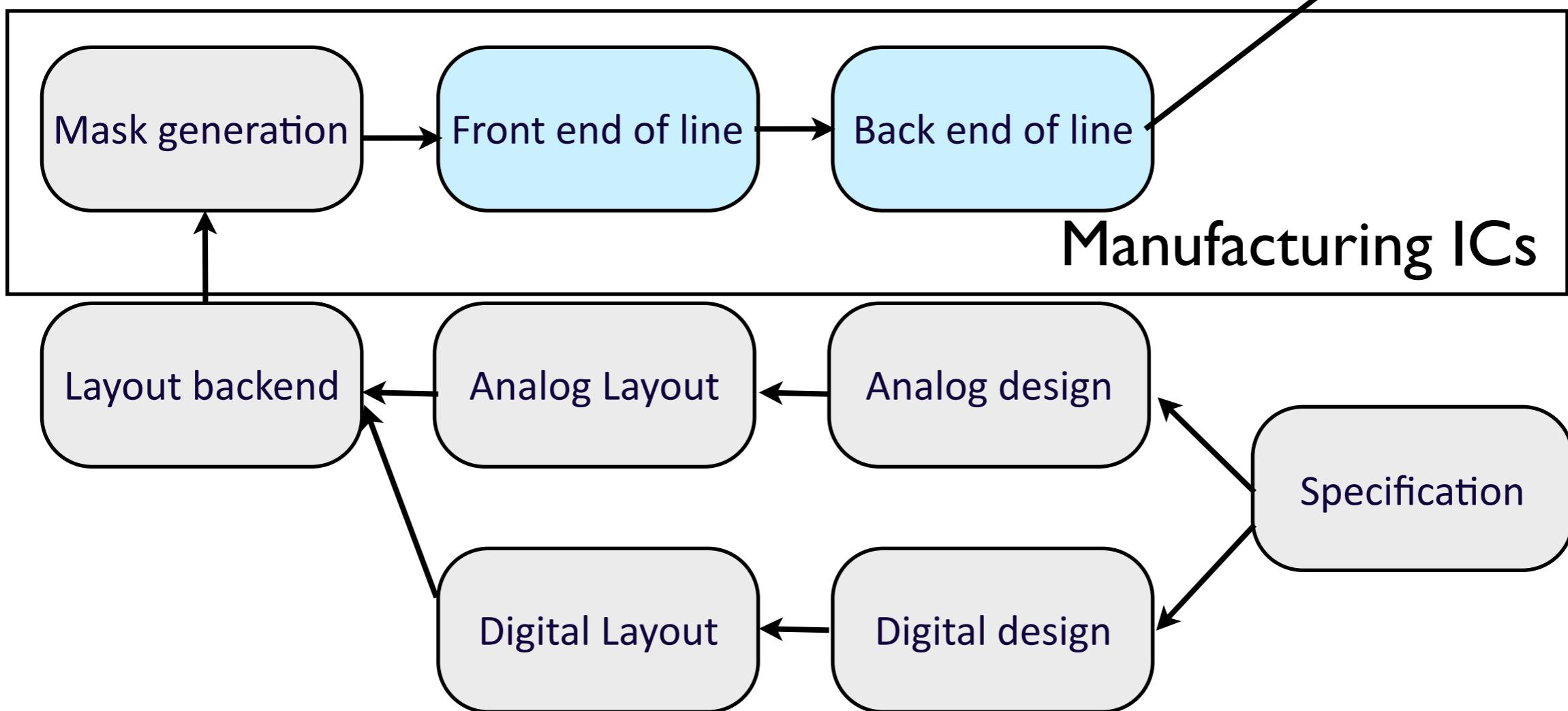


Making transistors

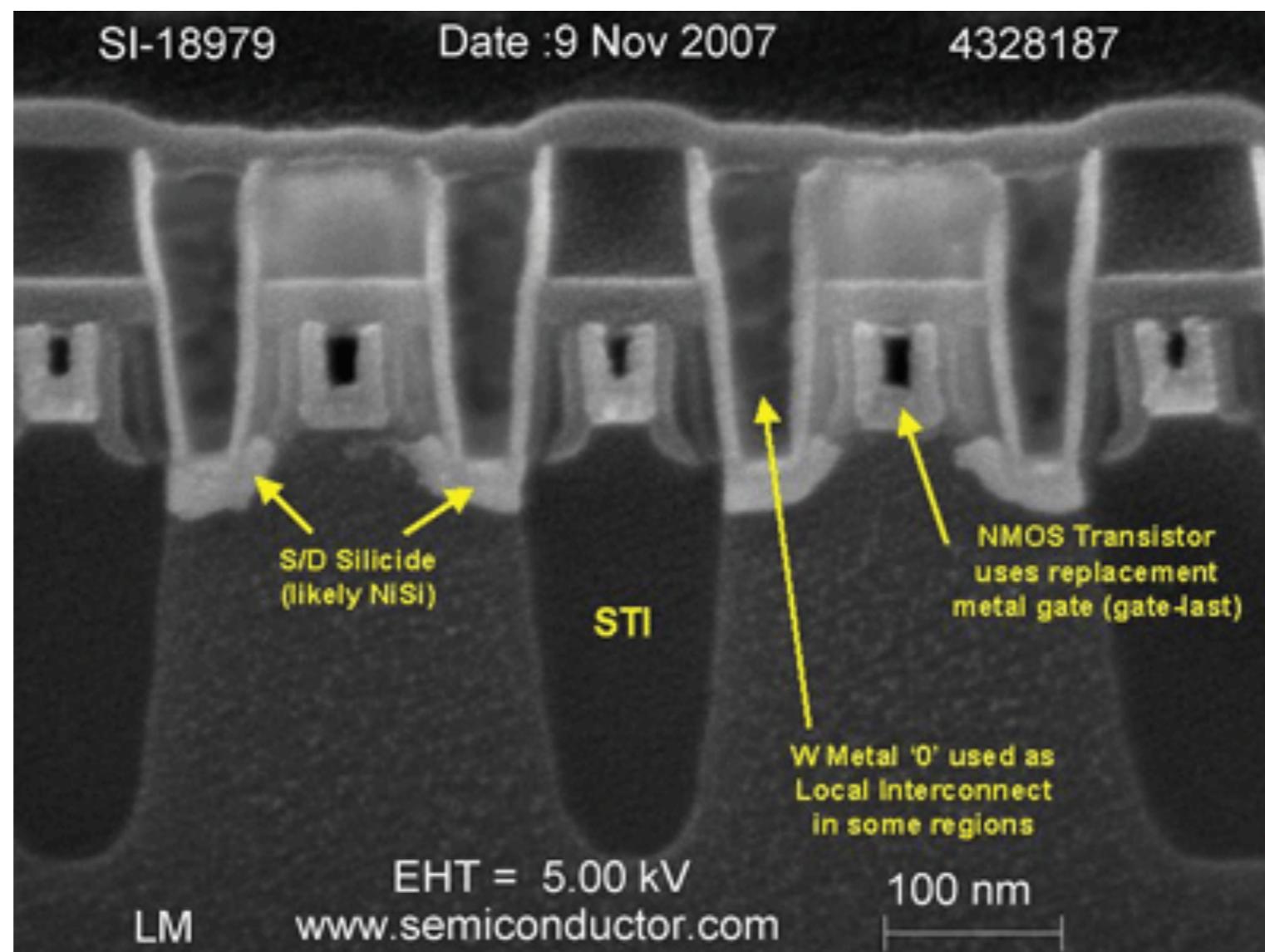


Nano-scale transistor

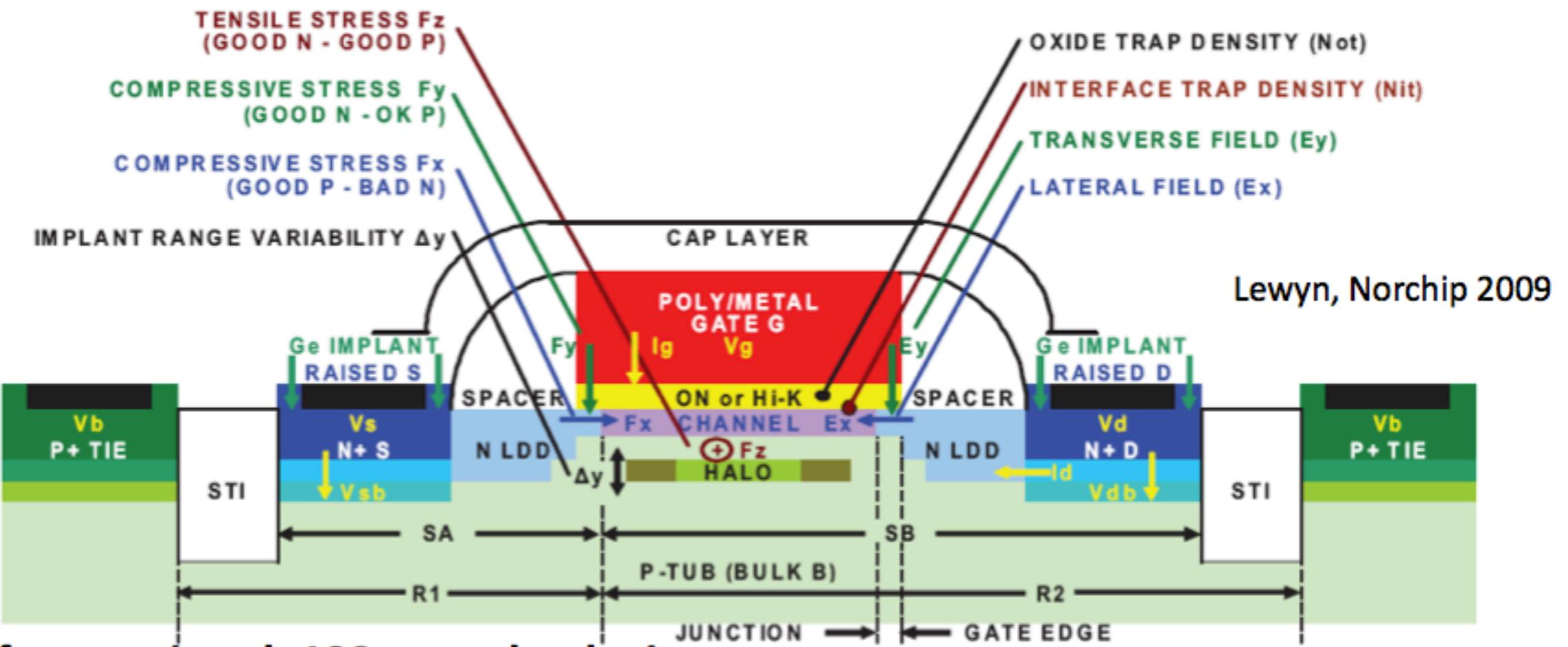


Photoresist and lithography

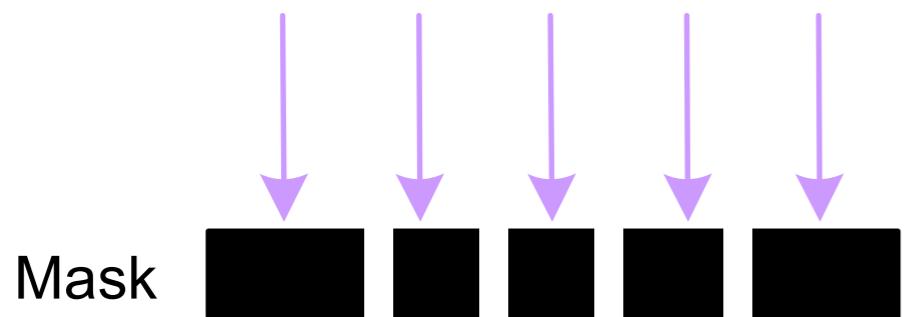

Mask

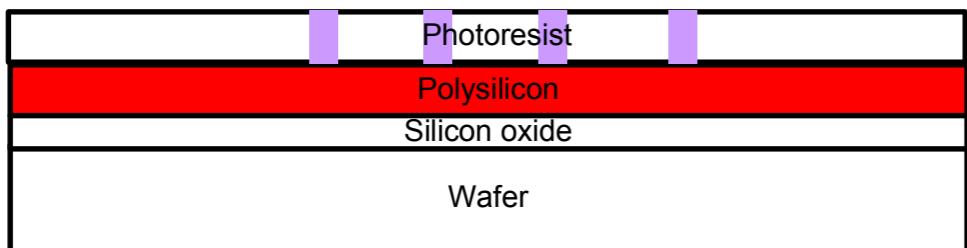


1) Expose photoresist

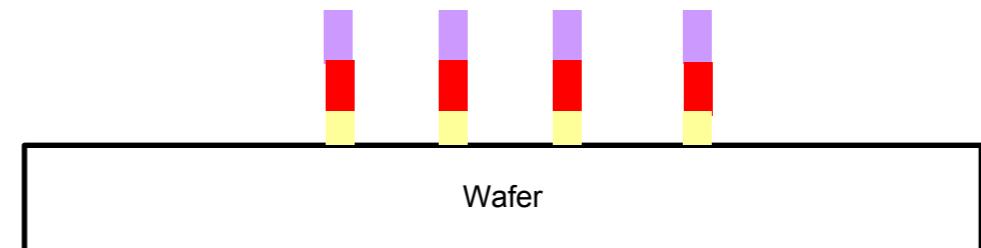


2) Remove photoresist and etch polysilicon

Doping and metal

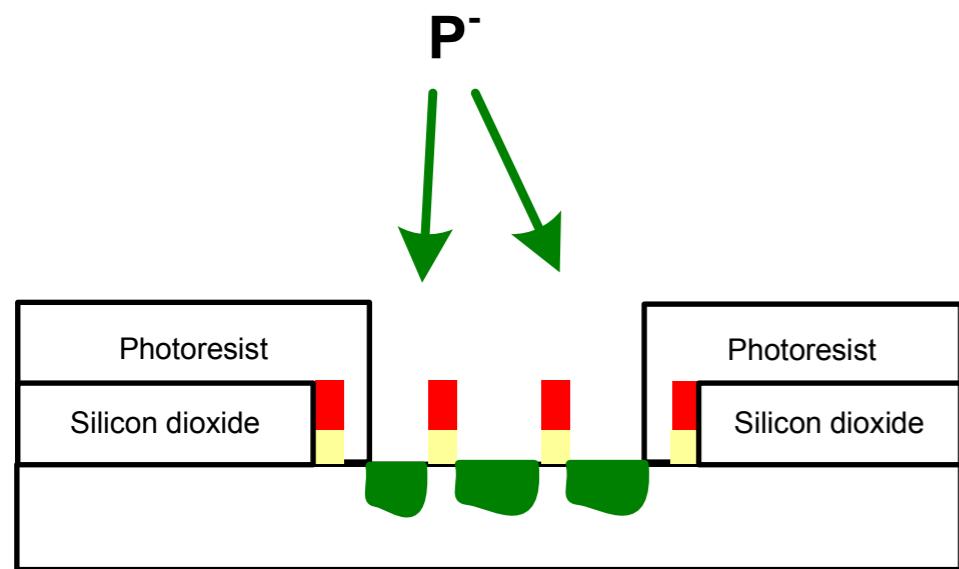


3) Add doping

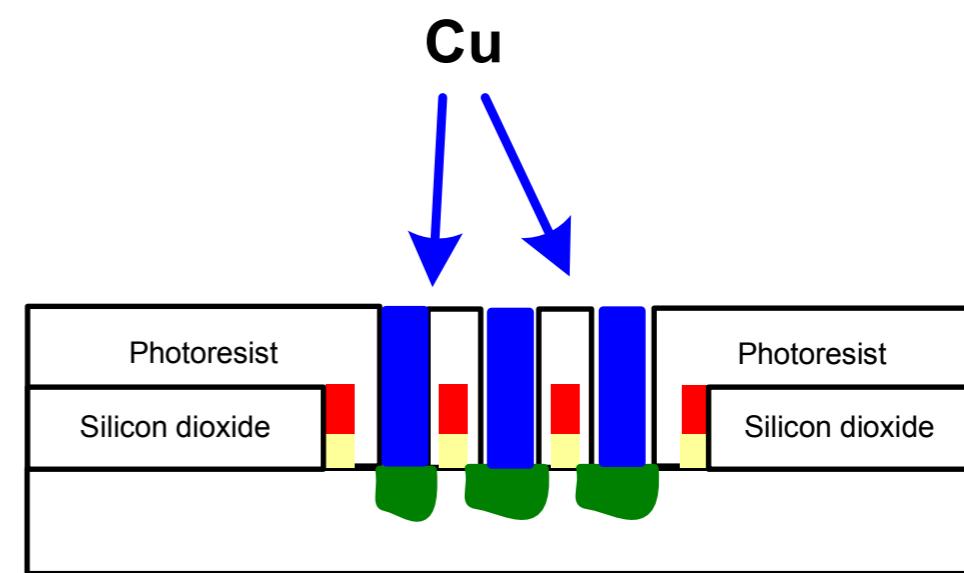

4) Add metal

Transistor

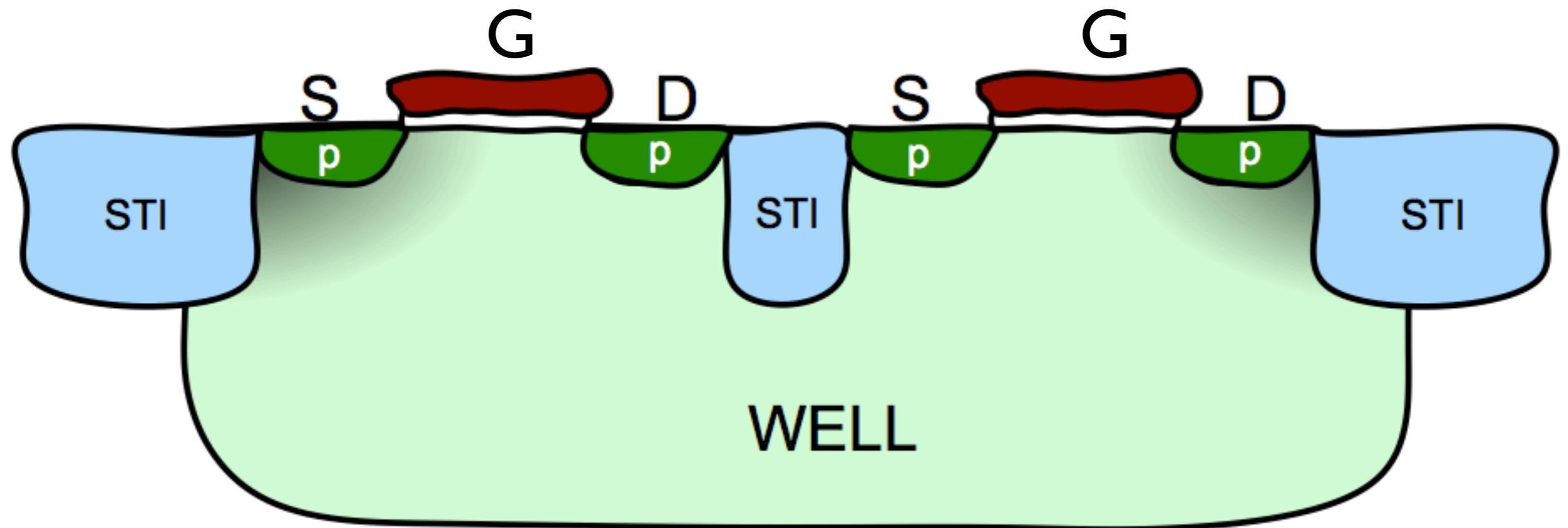

Topics not covered

- Simulation, corner verification
- Digital design (Verilog)
- System level design (Matlab)
- Project management
- Lab testing
- Writing documentation
- Writing patents

**What to focus on the
next five years**

Divide and conquer

- Break complex stuff into smaller pieces
- Ignore the difficult stuff, and try to get an approximate understanding, then add in the difficult stuff
- Don't be afraid if something is difficult
- Don't think you're stupid and won't be able to understand
- Don't think that everybody else is smarter than you

What you need to teach yourself

- Ability to work hard (constant speed)
- Ability to focus on the important stuff
- Programming
- Report writing
- Explaining things to other people

Lesson 2

Learn your courses, they are important

Things you should know about

- Software:
 - Schematic (Mentor graphics, Cadence, Synopsys, Tanner tools)
 - Layout (Mentor graphics, Cadence, Synopsys, Tanner tools)
 - Simulation (Eldo, Spectre, Hspice, BDA)
 - Scripting (Bash, Perl, Python, TCL, LISP)
 - Editors (Emacs)
 - Math software (Matlab, Maple, Octave)
- Information sources:
 - <http://ieeexplore.ieee.org>
 - <http://webcast.berkeley.edu/> (EE240 spring 2007 to spring 2010)